

MM10

(1) Cable constant

Primary: L, C

Secondary: V, Z

$$V = \frac{1}{\sqrt{LC}} \left[\frac{m}{s} \right]$$

$$Z_0 = \sqrt{\frac{L}{C}} \left[\Omega \right]$$


$$L = \frac{Z_0}{V} \left[\frac{H}{m} \right]$$

$$C = \frac{1}{V Z_0} \left[\frac{F}{m} \right]$$

(for loss free cable)

(sine) Solution for harmonic signals

New model

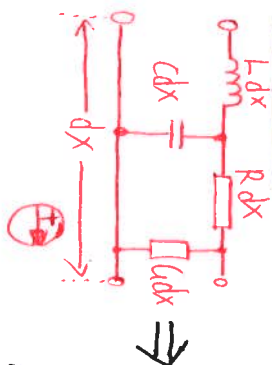

KS N



$$Z = R + j\omega L \left[\frac{\Omega}{m} \right]$$

$$Y = G + j\omega C \left[\frac{S}{m} \right]$$

Voltage on cable:

$$\frac{dV}{dx} = -Z I \left[\frac{V}{m} \right] \quad (1)$$

and current on cable:

$$\frac{dI}{dx} = -Y V \left[\frac{A}{m} \right] \quad (2)$$

$V(x)$ and $I(x)$ are KS N.

and Voltage and current on cable.

Add (1) and (2), we have:

$$\frac{d^2 V}{dx^2} = Z Y V \rightarrow \frac{d^2 V}{dx^2} = \gamma^2 V$$

This is one dimension wave equation

We define:

$$\gamma \triangleq \sqrt{ZY} = \alpha + j\beta \left[m^{-1} \right]$$

Propagation constant

where:

$$\alpha \left[Np/m \right]$$

attenuation constant

$$\beta \left[rad/m \right]$$

phase propagation constant

Neper (Np)

$$\text{Power } P = \frac{P_1}{P_2} \left[\cdot \right]$$

$$\text{Amplitude } A = \frac{A_1}{A_2} \left[\cdot \right]$$

$$P_{dB} = 10 \log P$$

$$A_{dB} = 20 \log A$$

$$A_{Np} = \ln A \quad (\text{i.e., } A = e^{A_{Np}})$$

$$1[Np] = e^{-1} = 2.718 \dots = 20 \cdot \log e \left[dB \right]$$

$$= 8.686 \left[dB \right]$$

(2) Lossless cable

We have $R = 0 \frac{\Omega}{m}$, $G = 0 \frac{S}{m}$

We get:

$$\gamma = \sqrt{ZY} = \sqrt{j\omega L \cdot j\omega C} = j\omega \sqrt{LC}$$

So

$$\alpha = 0 \quad \text{Np/m}$$

$$\beta = \omega \sqrt{LC} \quad [\text{rad/m}]$$

Solution:

$$V(x) = V^+(x) + V^-(x) = V^+ e^{-j\beta x} + V^- e^{+j\beta x} \quad [V]$$

$$I(x) = I^+(x) + I^-(x) = I^+ e^{-j\beta x} + I^- e^{+j\beta x} \quad [A]$$

$$= \frac{1}{Z_0} [V^+(x) - V^-(x)] \quad [A]$$

We have:

$$Z_0 = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{L}{C}} \quad [\Omega]$$

$$V = \sqrt{Z Y} \quad \left[\frac{V}{S} \right]$$

$$\beta = \omega \sqrt{ZY} = \frac{\omega}{v} \quad \left[\frac{\text{rad}}{m} \right] \quad \star$$

Note:

$$V^+(x) = V^+ e^{-j\beta x}$$

$V^+(x)$ is complex function.

$$V^+ = V^+(0)$$

complex constant

Wave propagation


We see from the incident wave:

$$V^+(x) = V^+ \cdot e^{-j\beta x}$$

$$\Rightarrow V^+ \cdot e^{-j\beta x} \cdot e^{j\omega t}$$

$$\rightarrow |V^+| \cdot \cos(\omega t - \beta x)$$

\Rightarrow for growing time t

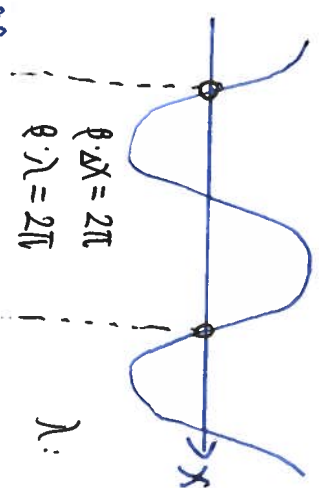


λ : wavelength [m]

where

$$\beta = \frac{\omega}{v} = \frac{2\pi}{\lambda} \Rightarrow \frac{2\pi}{\lambda} t = \frac{2\pi}{\lambda} \Rightarrow \frac{t}{\lambda} = \frac{1}{\lambda} \Rightarrow \lambda = \frac{v}{f} \quad \star$$

(3) Generalized Z and k

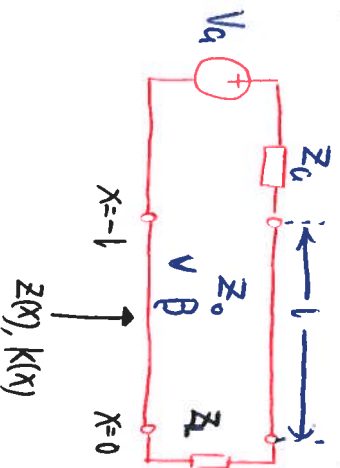

It is defined:

$$Z(x) \triangleq \frac{V(x)}{I(x)} = \frac{V^+(x) + V^-(x)}{I^+(x) + I^-(x)} = Z_0 \cdot \frac{V^+(x) + V^-(x)}{V^+(x) - V^-(x)}$$

$$= Z_0 \cdot \frac{1 + \frac{V^-}{V^+}}{1 - \frac{V^-}{V^+}} = Z_0 \cdot \frac{1 + k(x)}{1 - k(x)} \quad [\Omega] \quad (3)$$

Generalized Impedance

$$k(x) \triangleq \frac{V^-(x)}{V^+(x)} = \frac{V^- e^{-j\beta x}}{V^+ e^{-j\beta x}} = \frac{V^-(0)}{V^+(0)} \cdot e^{j2\beta x}$$

$$= k(0) \cdot e^{j2\beta x} = k(0) e^{-j2\beta l} \quad [\cdot]$$

~~amplitude is not changed with X.~~

When $k(0) = k_L$, we have: $k(x) = k_L \cdot e^{j2\beta x}$

amplitude is not changed with X .

From (3), we also have:

$$k(x) = \frac{Z(x) - Z_0}{Z(x) + Z_0} \quad [\cdot]$$

For $x=0$,

$$k_L = \frac{Z_L - Z_0}{Z_L + Z_0} \quad [\cdot]$$

where, $Z(0) = Z_L$ and $k(0) = k_L$

We also have:

$$k(x) = \frac{V^-(x)}{V^+(x)} = -\frac{I^-(x)}{I^+(x)} \quad [\cdot]$$


$$Z(x) = \frac{V(x)}{I(x)}$$

$$Z_0 = \frac{V^+(x)}{I^+(x)}$$

$$V(x) = V^+(x) (1 + k(x))$$

$$I(x) = I^+(x) (1 - k(x))$$

Input impedance

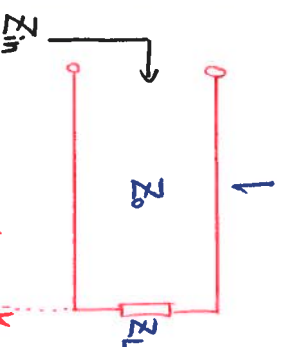


$$k_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$k(-1) = k_L \cdot e^{-j2\beta l}$$

$$Z_{in}(x=-1) = Z_0 \cdot \frac{1 + k(-1)}{1 - k(-1)} \quad [\Omega]$$

Further calculations

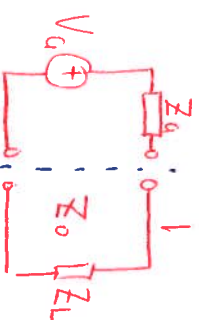

$$V(-1) = V_a \cdot \frac{Z(-1)}{Z_a + Z(-1)}$$