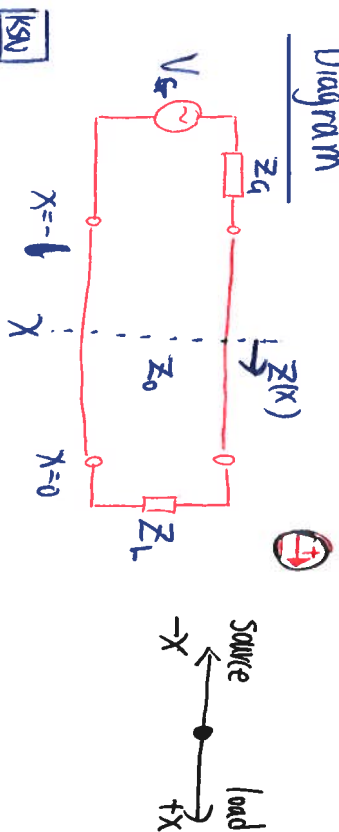


(1) Transmission line model

Diagram



Formula (Generalized k and Z):

$$k(x) = \frac{Z(x) - Z_0}{Z(x) + Z_0} \quad [\cdot] \quad Z(x) = Z_0 \frac{1+k(x)}{1-k(x)} \quad [\Omega]$$

$$k(0) = k_L = \frac{Z_L - Z_0}{Z_L + Z_0} \quad [\cdot] \quad Z(0) = Z_L = Z_0 \frac{1+k_L}{1-k_L} \quad [\Omega]$$

$$k(x) = k_L \cdot e^{j2\beta x}$$

Smith chart

We see that:

$$k(x) \leftrightarrow Z(x)$$

$k(x)$ and $Z(x)$ are complex functions.

So we can express the functions as:

$$Z(x) = R(x) + jX(x) \quad [\Omega]$$

$$k(x) = U(x) + jV(x) \quad [\cdot]$$

Normalize $Z(x)$ with Z_0

$$Z_n = \frac{Z(x)}{Z_0} = r(x) + jx(x) \quad [\cdot]$$


For reflection coefficient

$$k(x) = \frac{Z(x) - Z_0}{Z(x) + Z_0} = \frac{Z(x)/Z_0 - 1}{Z(x)/Z_0 + 1} = \frac{Z_n - 1}{Z_n + 1} \quad [\cdot]$$


and reversely

$$Z_n = \frac{1+k}{1-k} \quad [\cdot]$$

(2) Smith chart's construction

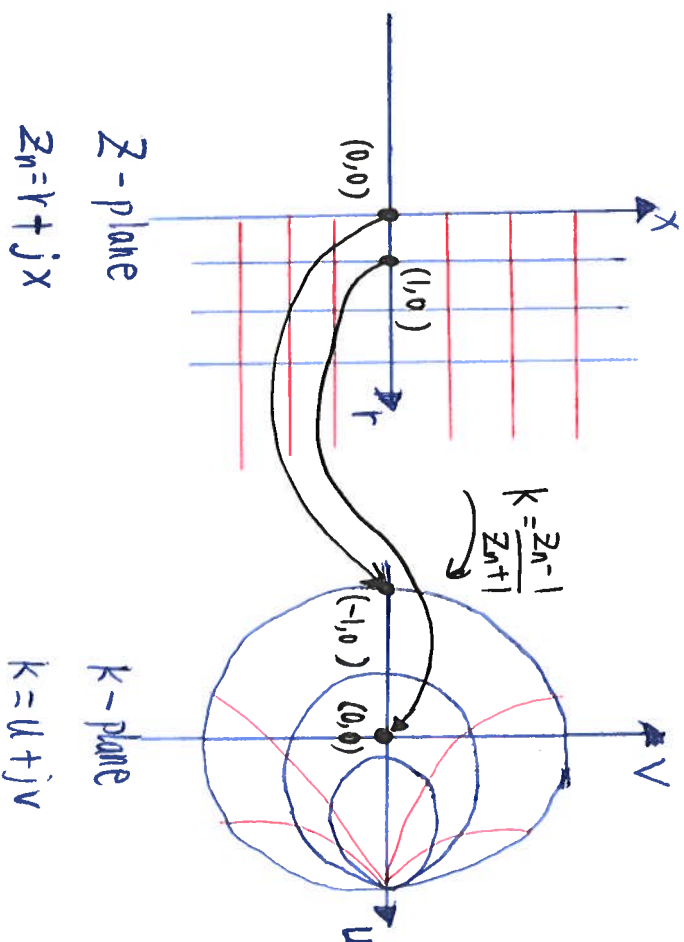

Significant points and curves

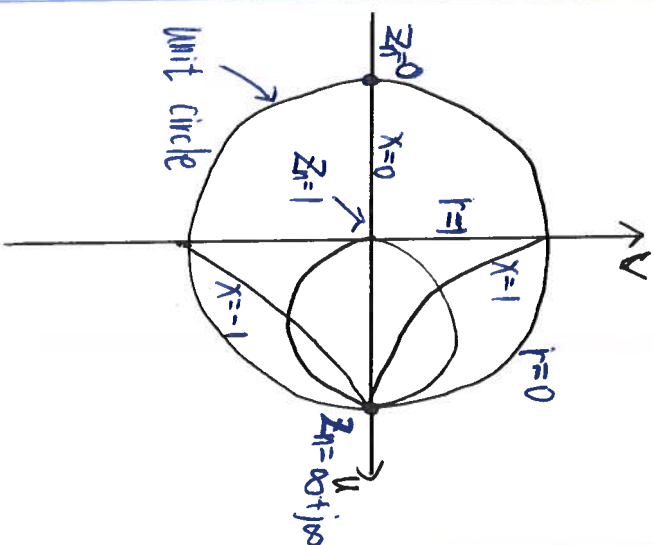


Turn around smith chart

$$K(x) = K_L \cdot (e^{j2\theta x})$$

$$= K_L \cdot (1 \angle 2\theta x)$$

$$= K_L \cdot (1 \angle 2\pi \frac{x}{\lambda_2}) \quad [\cdot]$$

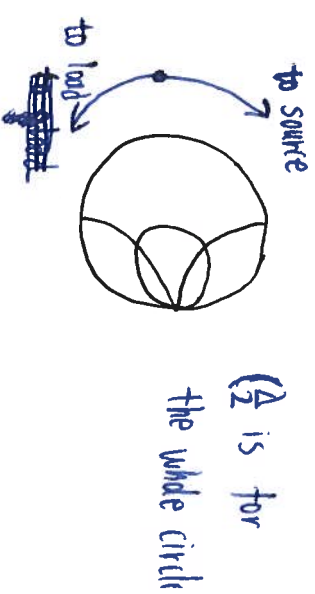(where $2\theta x = 2 \cdot \frac{2\pi}{\lambda} x = 2\pi \cdot \frac{x}{\lambda_2}$)



(3) Admittance chart


For admittance, we can see

$$Y_n = \frac{1}{Z_n} = \frac{Z_o}{Z(x)} = \frac{Y(x)}{Y_o} = \frac{1-k}{1+k} = \frac{1+k}{1-(-k)}$$

where $Y_o = \frac{1}{Z_o}$ and $Y(x) = \frac{1}{Z(x)}$


If $k' = -k$,

$$Y_n = \frac{1+k'}{1-k'}$$

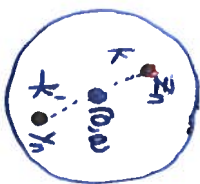

Mirror according to (0,0)
(either)

Z- and Y-chart

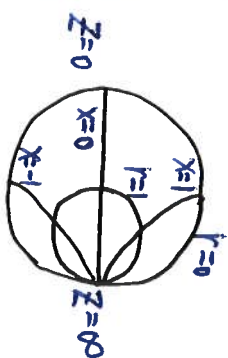


Z-chart

$$Z_n = r + jx$$

where

r is resistance

x is reactance

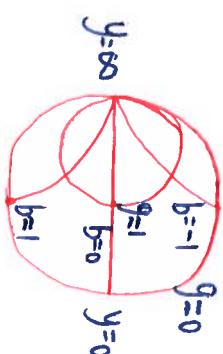

Y-chart

$$Y_n = g + jb$$

g is conductance


b is susceptance

(14) Single stub impedance transformer

Example:

$$Z_0 = 50 \Omega$$

$$Z_L = 100 - j80 \Omega$$

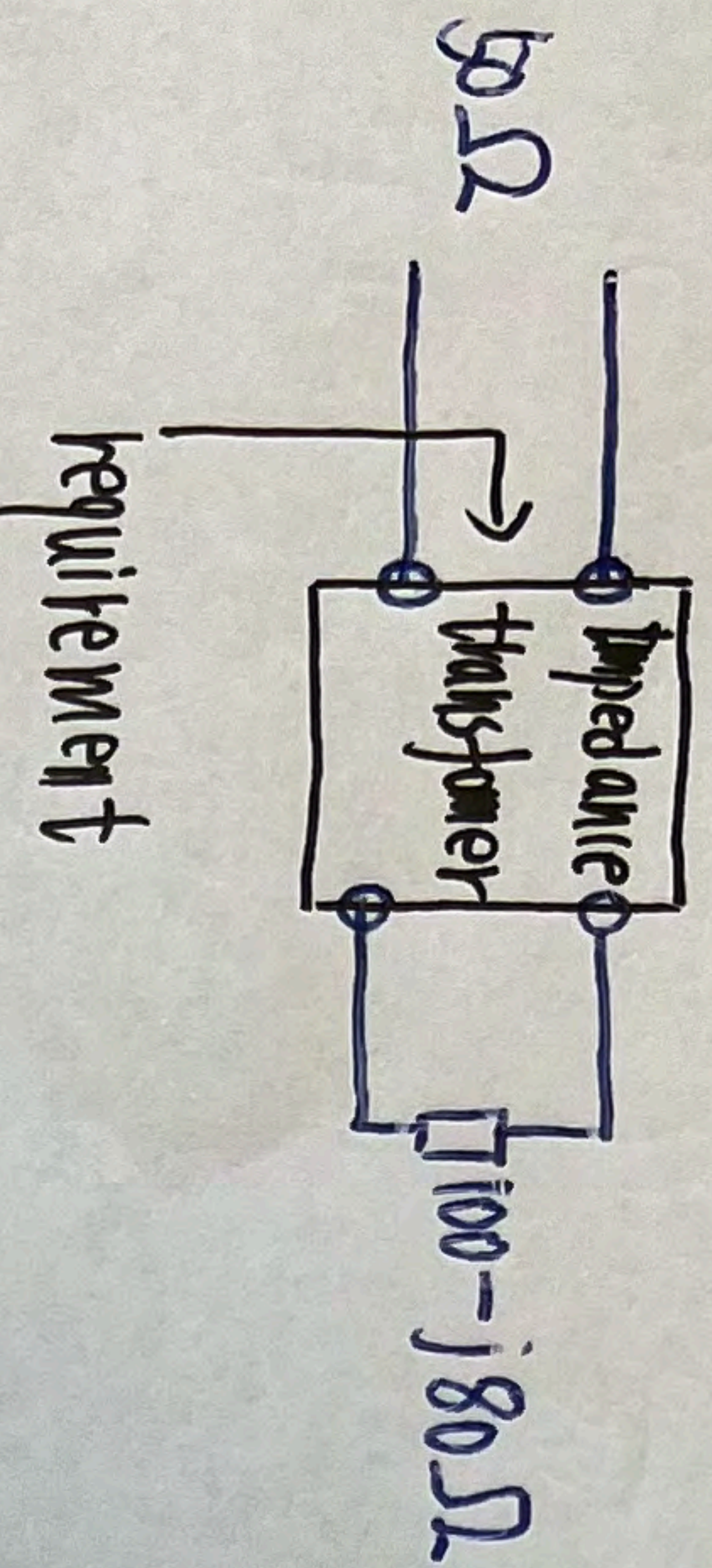


$$Z_{in} = Z_0 = 50 \Omega$$


$$\text{or } k = 0$$

$$\text{or } Z_n = 1 + j0 = 1$$
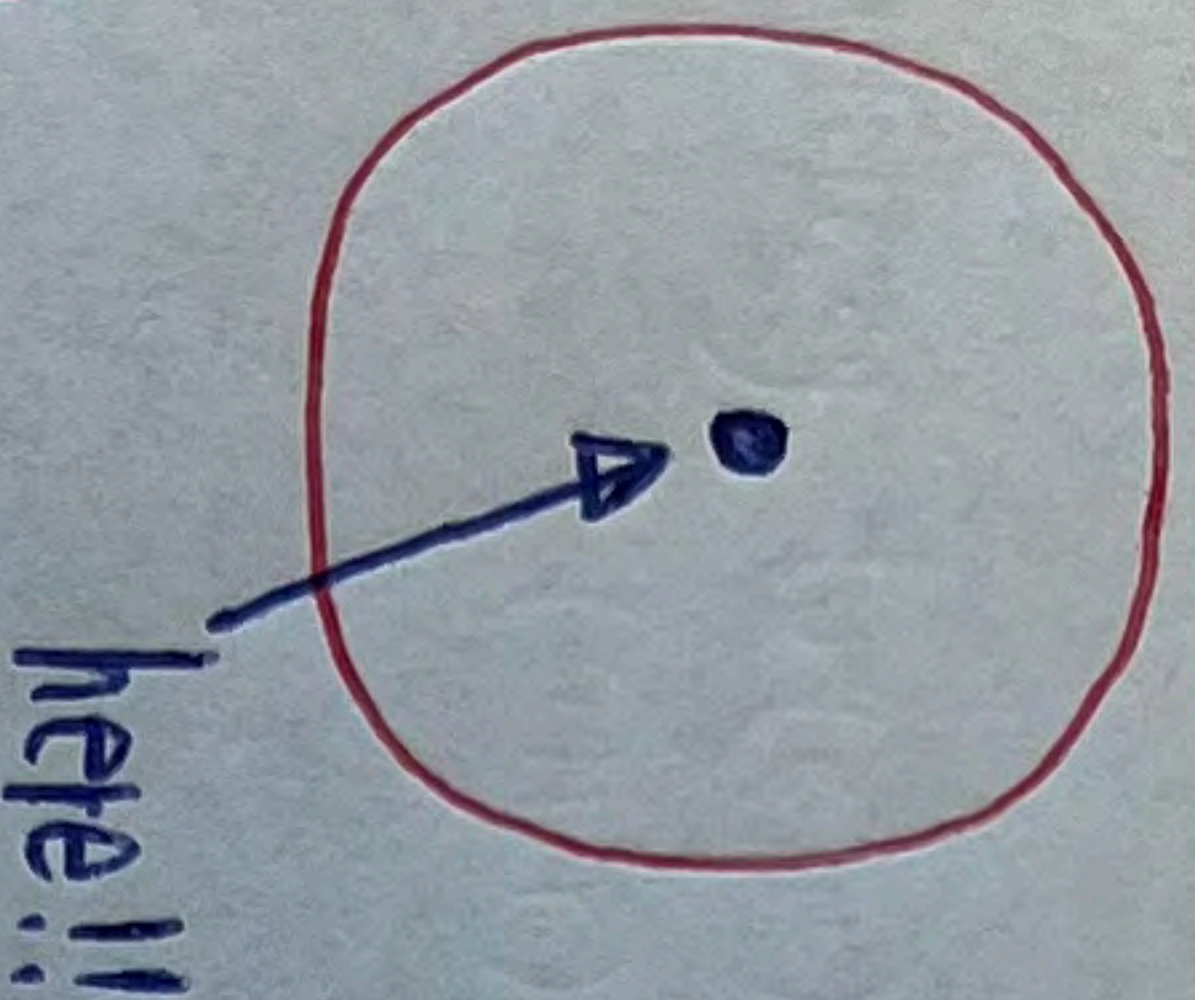
$$\text{or } Y_n = 1 + j0 = 1 \quad (g=1, b=0)$$



Solution

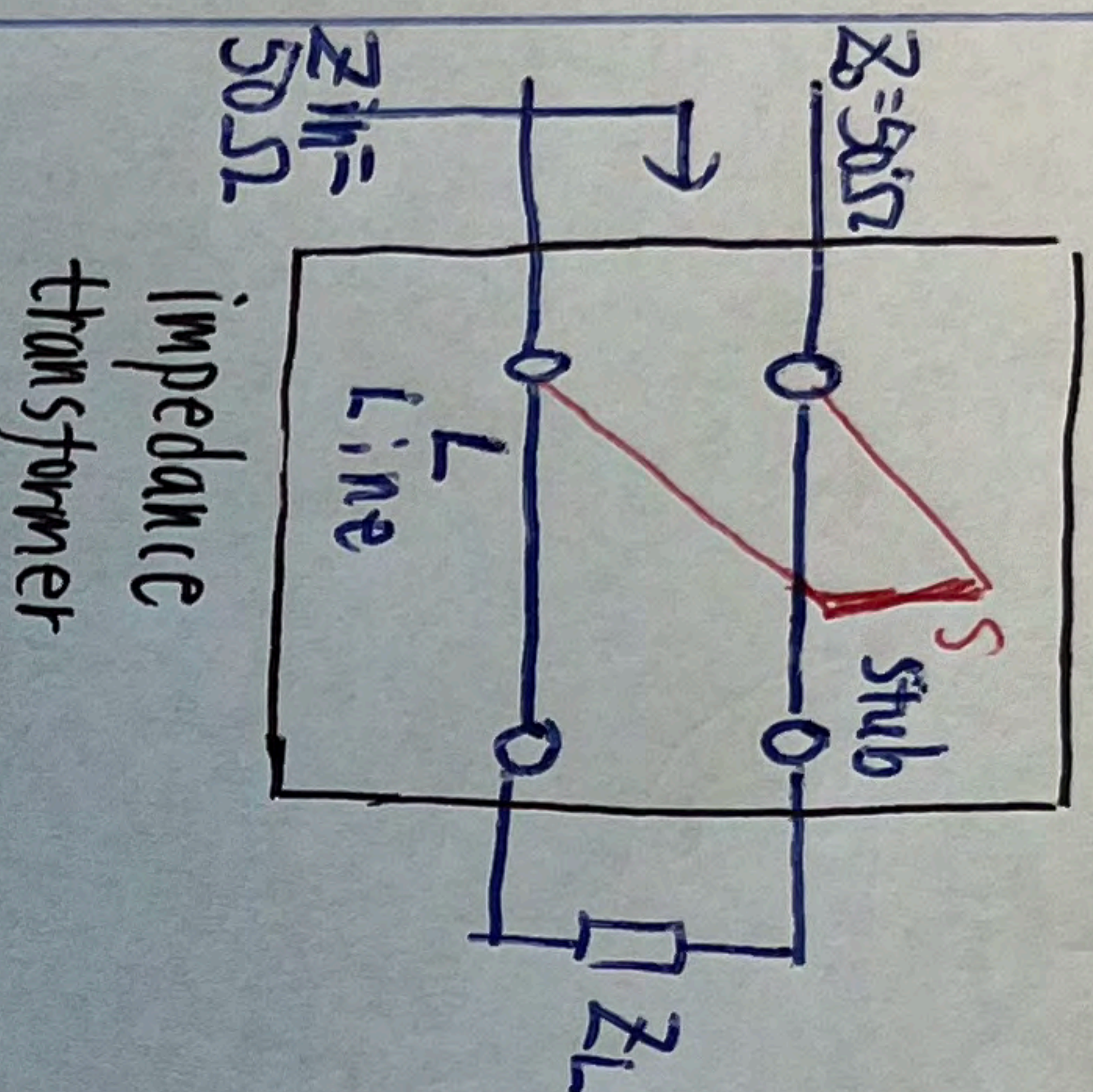


Steps

① Normalize Z_L


$$Z_n = \frac{Z_L}{Z_0} = \frac{100 - j80}{50} = 2 - j1.6$$

② Find the admittance Y_n of Z_n

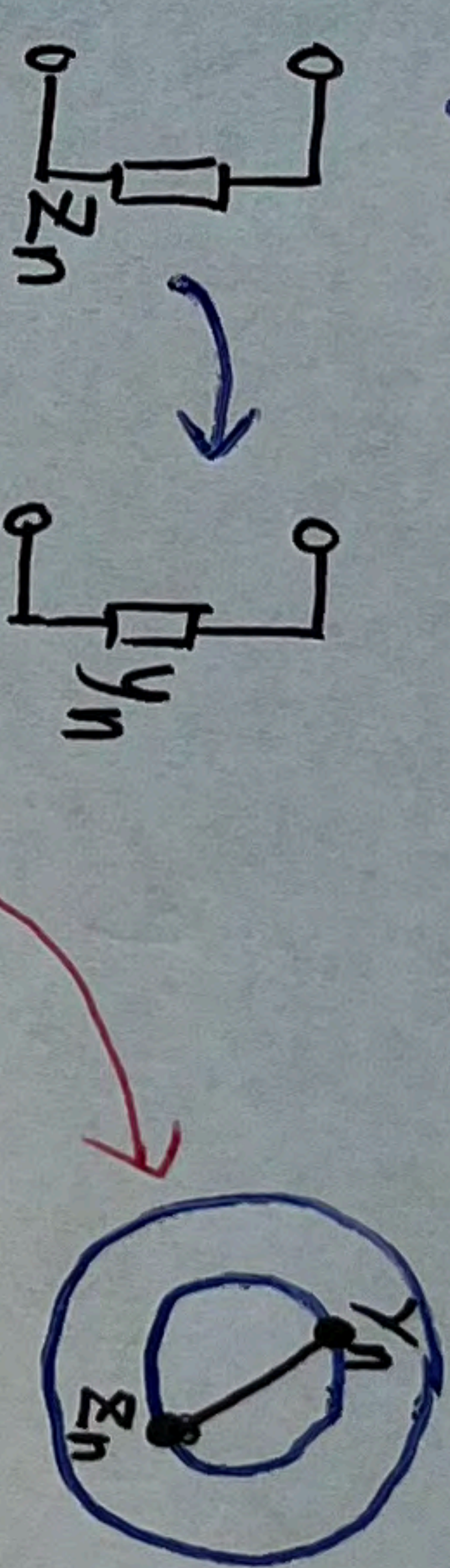


The chart is Y-chart now!!

③ Insert line L until $g=1$

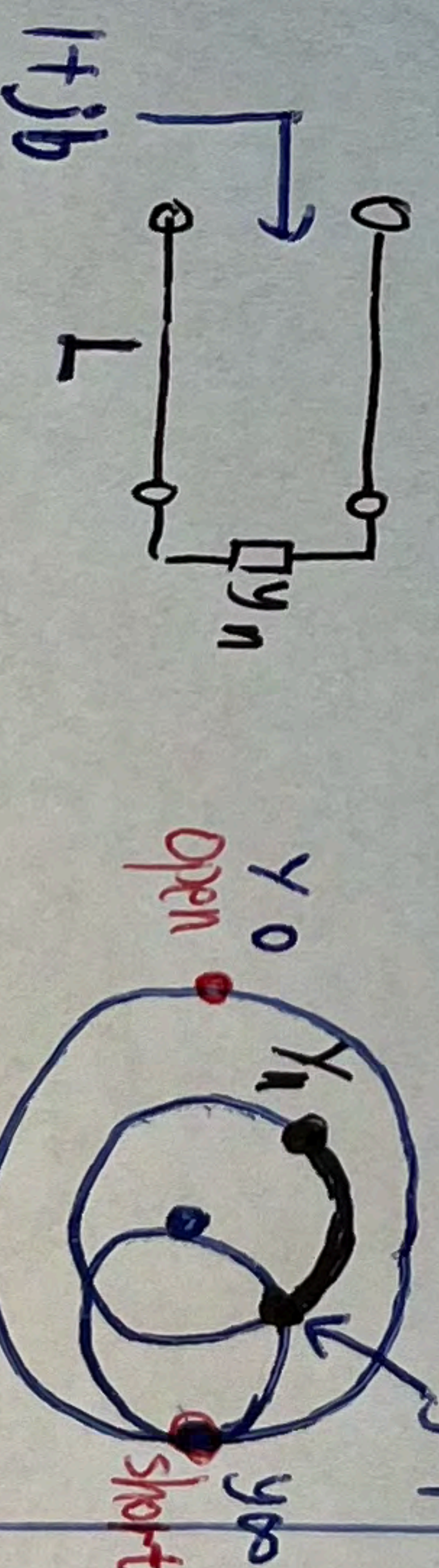

④ Mount a stub of $-jb$ in parallel.

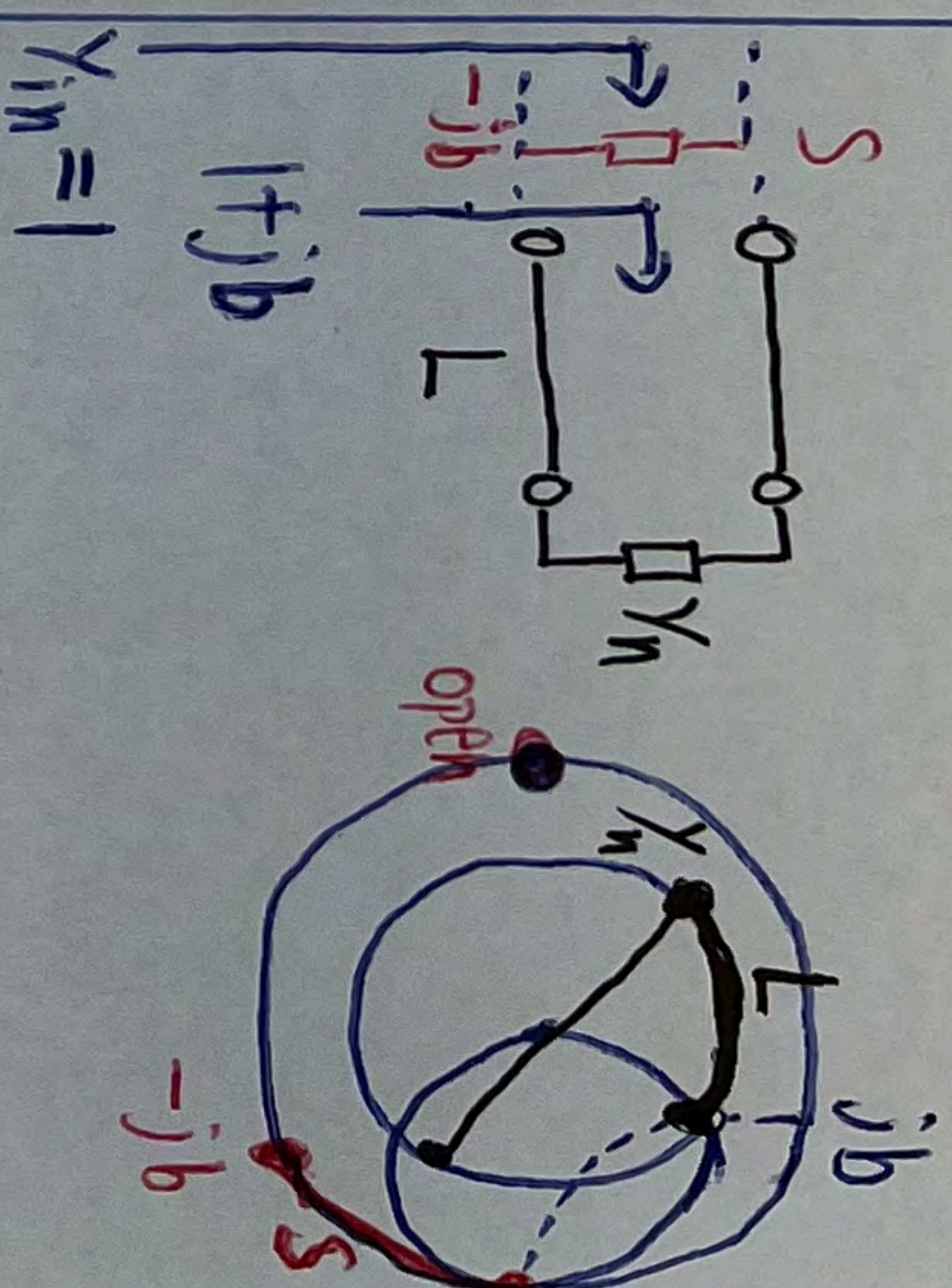

Solution

