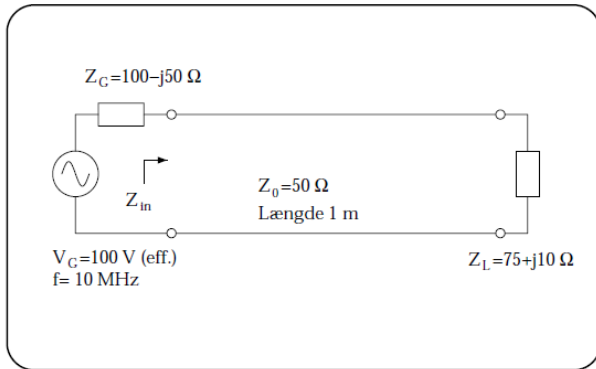


Exercise 10.1

Calculate the following quantities for the setup shown in the figure below, and provide them with the correct units. The cable is 1 m long. It is lossless, and the phase propagation constant is $1.5 \pi \text{ rad/m}$.



- Calculate K_L in polar form.
- Calculate the reflection coefficient $K(-l)$ in polar form.
- Calculate the input impedance Z_{in} in rectangular form.
- Calculate the voltage at the input of the cable.
- Calculate the current flowing into the cable.
- Now, remove the generator including the generator impedance. Calculate which component should be connected at the input of the cable to make the impedance purely real.