

# High-Speed Electronics in Practice

SHUAI ZHANG

SELMA LAGERLOFS VEJ 312


9220 AALBORG ØST

(sz@es.aau.dk)

# High-Speed Electronics in Practice

## **MM13. Cable Models and Power Ratio**

# Recall

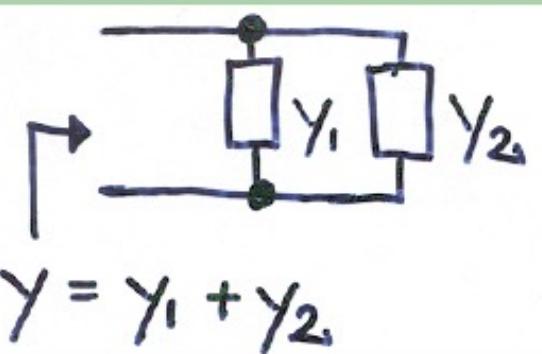

Admittancer


Single Stub  
Impedance  
Transformer

Steps

① Normalize  $Z_L$



$$Z_n = \frac{Z_L}{Z_0} = \frac{100 - j80}{50} = 2 - j1.6$$

② Find the admittance  $Y_n$  of  $Z_n$

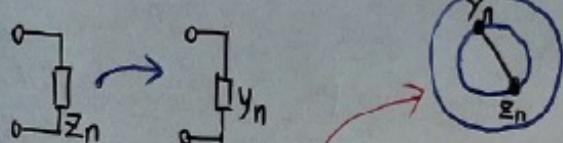


The chart is Y-chart now!!


③ Insert line  $L$  until  $g=1$

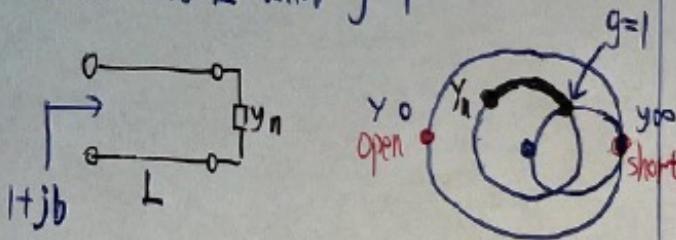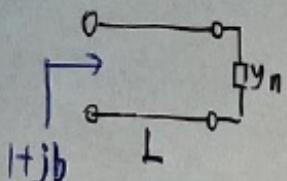


④ Mount a stub of  $-jb$  in parallel.

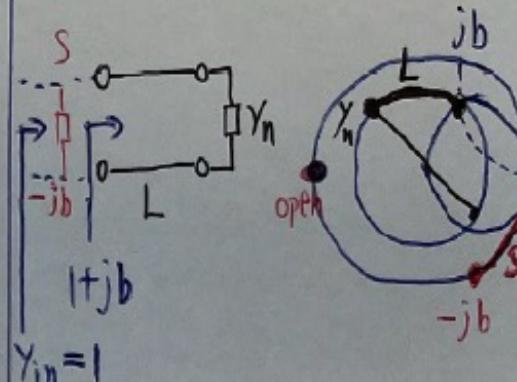


Solution

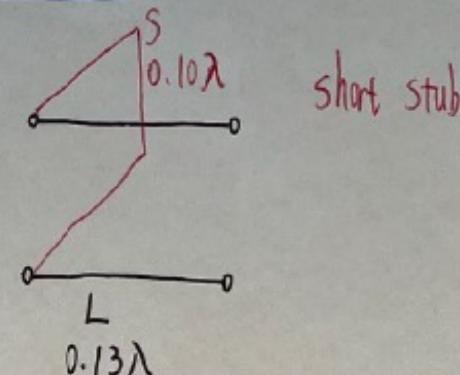


# Recall

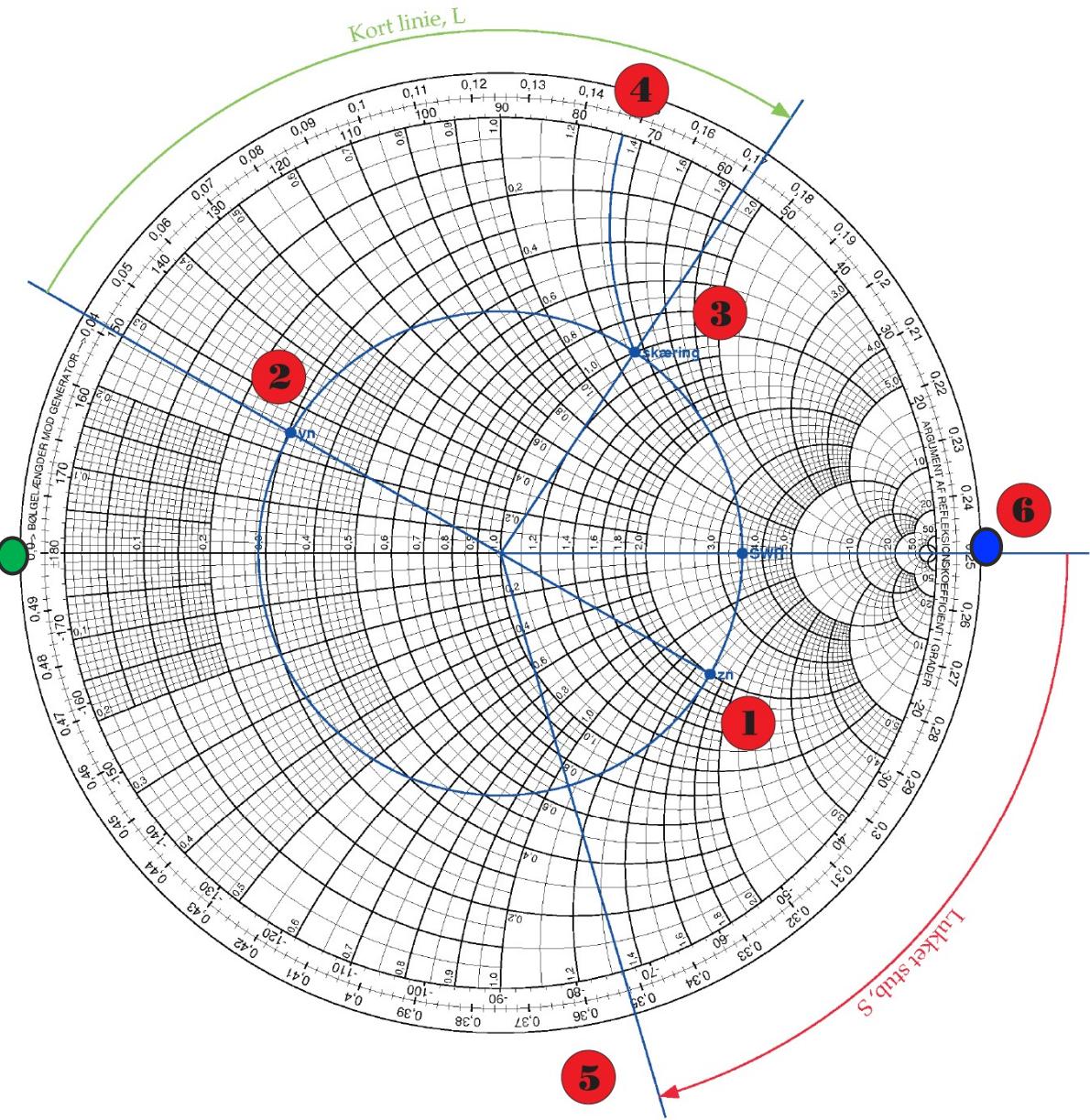

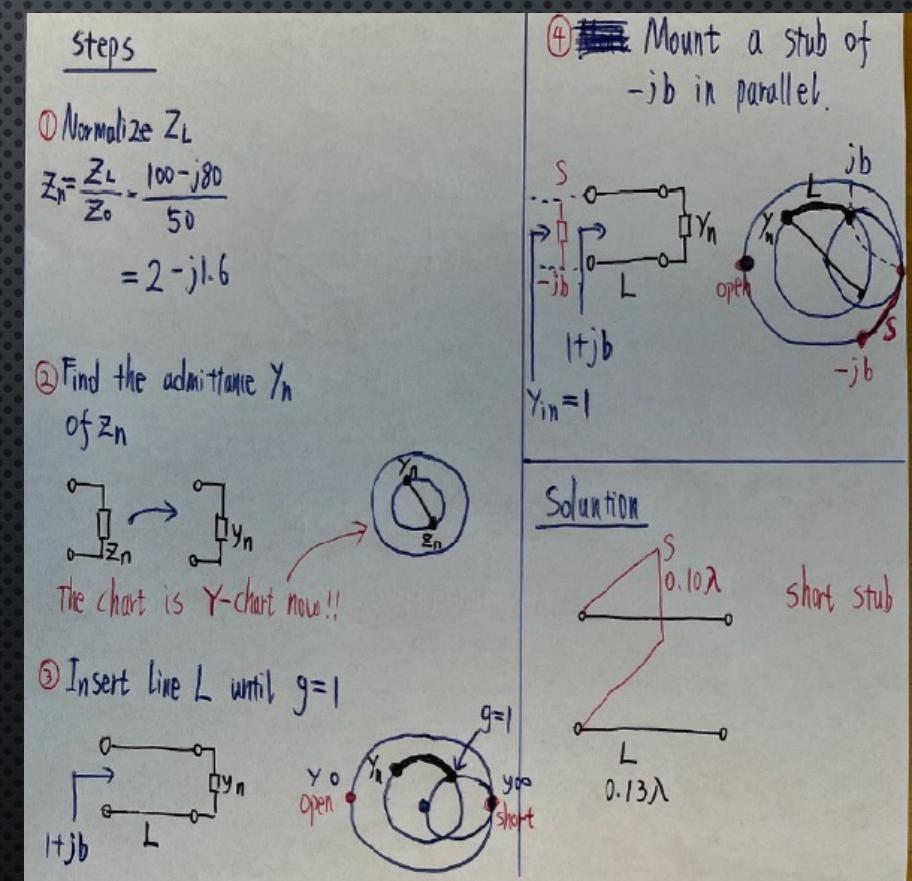1. Rotate clockwise (from load to source direction).
2. It is admittance now. If it is short-circuit stub, start from blue point. If it is open-circuit stub, start from green point.




# Recall

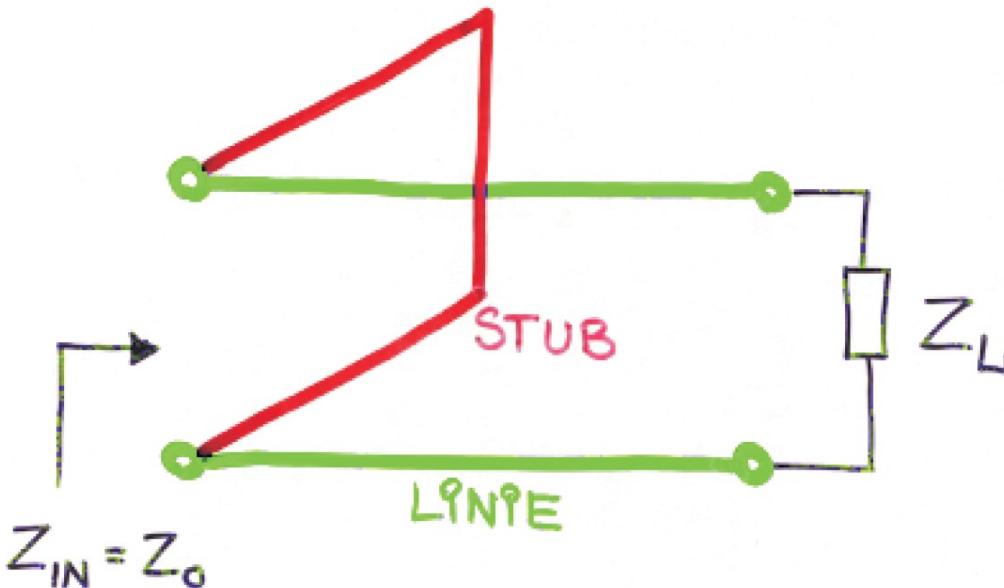

Single Stub  
Impedance  
Transformer

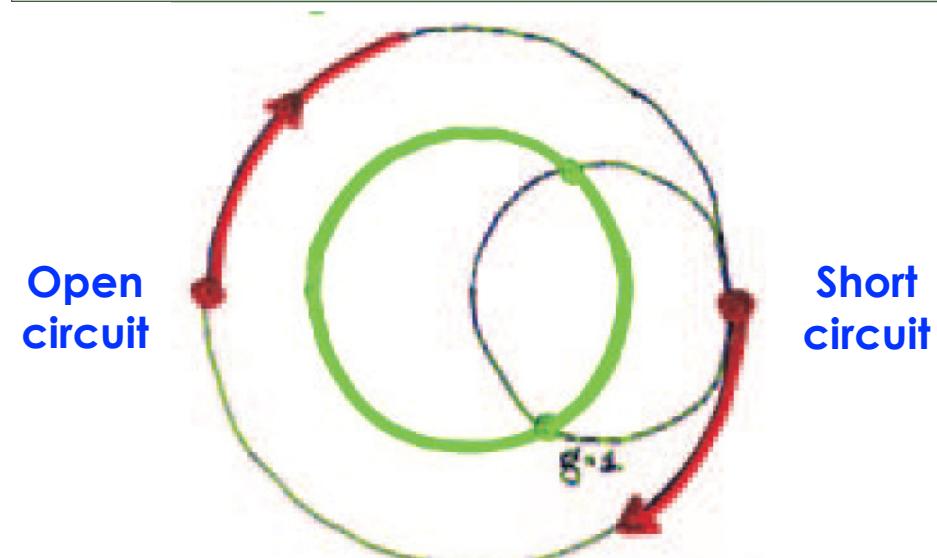- There are always 4 solutions:
1. Short line, open-circuit stub
  2. Short line, short-circuit stub
  3. Long line, open-circuit stub
  4. Long line, short-circuit stub




# Recall

## CIRKLER I SMITHKORTET

Smith chart  
with other information

Gonzales, G.:  
Microwave Transistor Amplifiers, 2. ed.  
Prentice Hall, 1997  
ISBN 0-13-254335-4  
Fig. 4.3.3 page 302

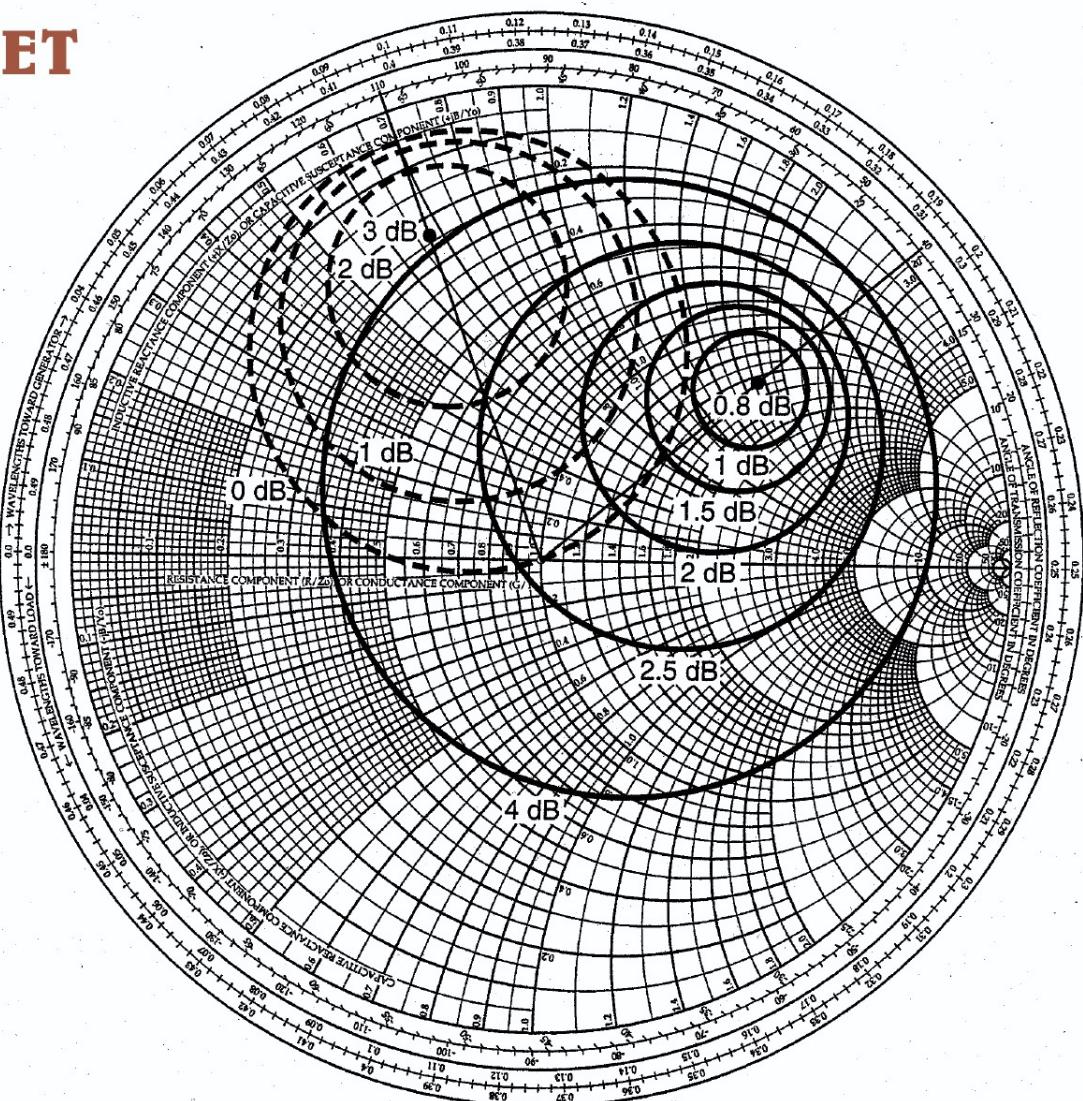

**Figure 4.3.3** Noise figure circles (solid curves) and  $G_s$  constant-gain circles (dashed curves). The transistor is a GaAs FET with  $V_{DS} = 4$  V,  $I_{DS} = 12$  mA, and  $f = 6$  GHz.

# CABLE MODELS AND POWER RATIO

Targets:

1. Read “Grundlæggende Transmissionsledningsteori” (Page 38-44, 46-48, 93-100) (before or after the lecture)
2. Be able to calculate with cable model and power calculation in KSN (lecture)
3. Finish the exercise (after the lecture)

# Transmissionline Cable Models for Calculations

1. Calculate between the primary and secondary cable constant

$$\mathbf{L}, \mathbf{C}, \mathbf{R}, \mathbf{G} \leftrightarrow Z_0, \gamma$$

2. Calculate  $K_L$  from  $Z_0$  and  $Z_L$

3. Calculate between the impedance and reflection coefficient.

$$K(x) \leftrightarrow Z(x)$$

4. Calculate voltage and current

$$V(x), I(x), V^+(x), V^-(x), I^+(x), I^-(x)$$

5. Calculate transmission and loss power

$$P_{\text{TRANS}}(x), P_{\text{TAB}}(x)$$

# Calculations with Lossy Cables

Neper:

$$A_{N_p} \triangleq [\ln A \quad [N_p]]$$

where  $A = \frac{V_1}{V_2}$  or  $\frac{I_1}{I_2} [\cdot]$

$$| N_p = 20 \log e \text{ dB} = 8.686 \text{ dB}$$

$$(e \approx 2.72)$$

EXAMPLE:

22 mm coax med helix isolation

37 dB/km @ 200MHz

RG-8/U

88 dB/km @ 200MHz

70 dB/km @ 100 MHz

4 dB/km @ 1 MHz

$$88 \text{ dB/km} = 10,1 \text{ Np/km} = 0,0101 \text{ Np/m}$$

$$4 \text{ dB/km} = 0,46 \text{ Np/km} = 0,0005 \text{ Np/m}$$

# Calculations with Lossy Cables


SMITH CHART WITH LOSSY CABLE

$$k(x) = \frac{V^-(x)}{V^+(x)} = \frac{V^-}{V^+} \cdot e^{2j\gamma x}$$
$$= k_L \cdot e^{2dx} \cdot e^{2j\theta x} [.]$$

For  $x=-\infty$  ( $l=\infty$ ), we have

$$k(-l) \rightarrow 0$$

$$Z(-l) \rightarrow Z_0$$

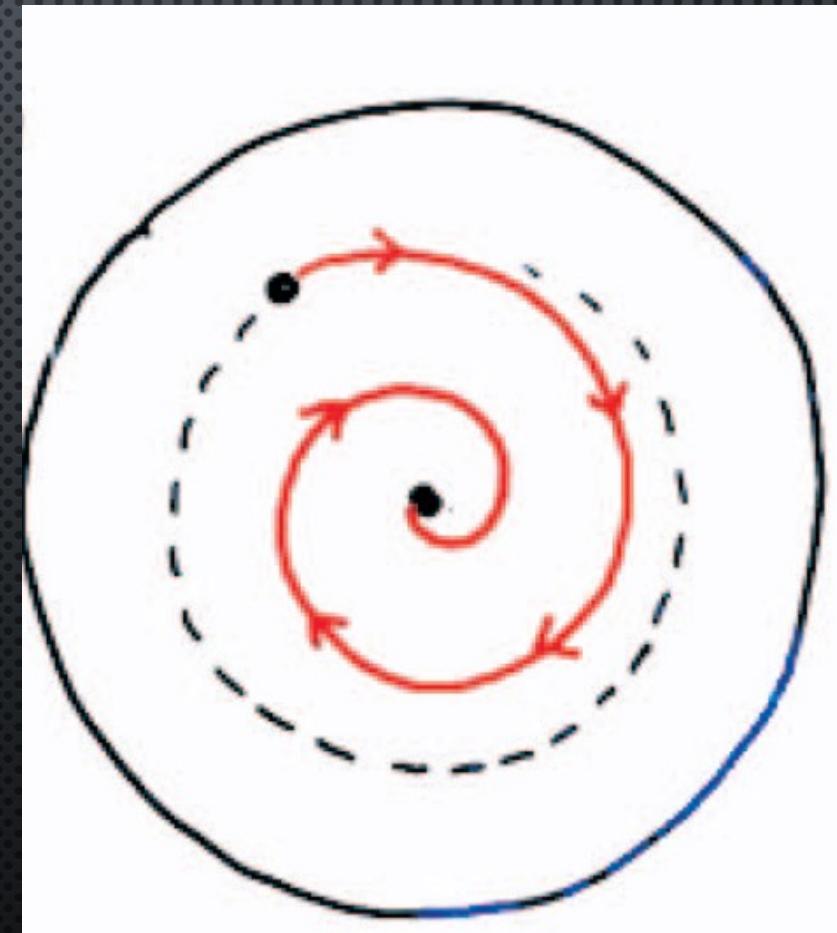

# Power Calculations in KSN with Lossy Cables

Blackboard (3)

## Instantaneous power

$$\begin{aligned} P_{\text{OBJEK}}(t) &\triangleq V(t) \cdot I(t) \\ &= V \cos(\omega t + \varphi) \cdot I \cos(\omega t + \theta) \\ &= \frac{1}{2} \cdot (VI \cos(\varphi - \theta)) + \frac{1}{2} (VI \cos(2\omega t + \varphi + \theta)) \end{aligned}$$

## Average power

$$P_{\text{MIDDEL}} \triangleq \frac{1}{T} \int_{t_0}^{t_0+T} P_{\text{OBJEK}}(t) dt = \frac{1}{2} VI \cos(\varphi - \theta)$$

## Average power

$$P_{\text{MIDDEL}} \triangleq \frac{1}{T} \int_{t_0}^{t_0+T} P_{\text{OBJEK}}(t) dt = \frac{1}{2} VI \cos(\varphi - \theta)$$

## Power in KSN


$$\begin{aligned} P_{\text{MIDDEL}} &= \frac{1}{2} \cdot \text{Re} [V \cdot I^*] \\ &= \frac{1}{2} \cdot \text{Re} [V e^{j\varphi} \cdot I e^{-j\theta}] \\ &= \frac{1}{2} \cdot \text{Re} [VI e^{j(\varphi - \theta)}] \\ &= \frac{1}{2} VI \cos(\varphi - \theta) \end{aligned}$$

SAMME

The power in KSN is actually the power in time average.


# Power Calculations in KSN with Lossy Cables
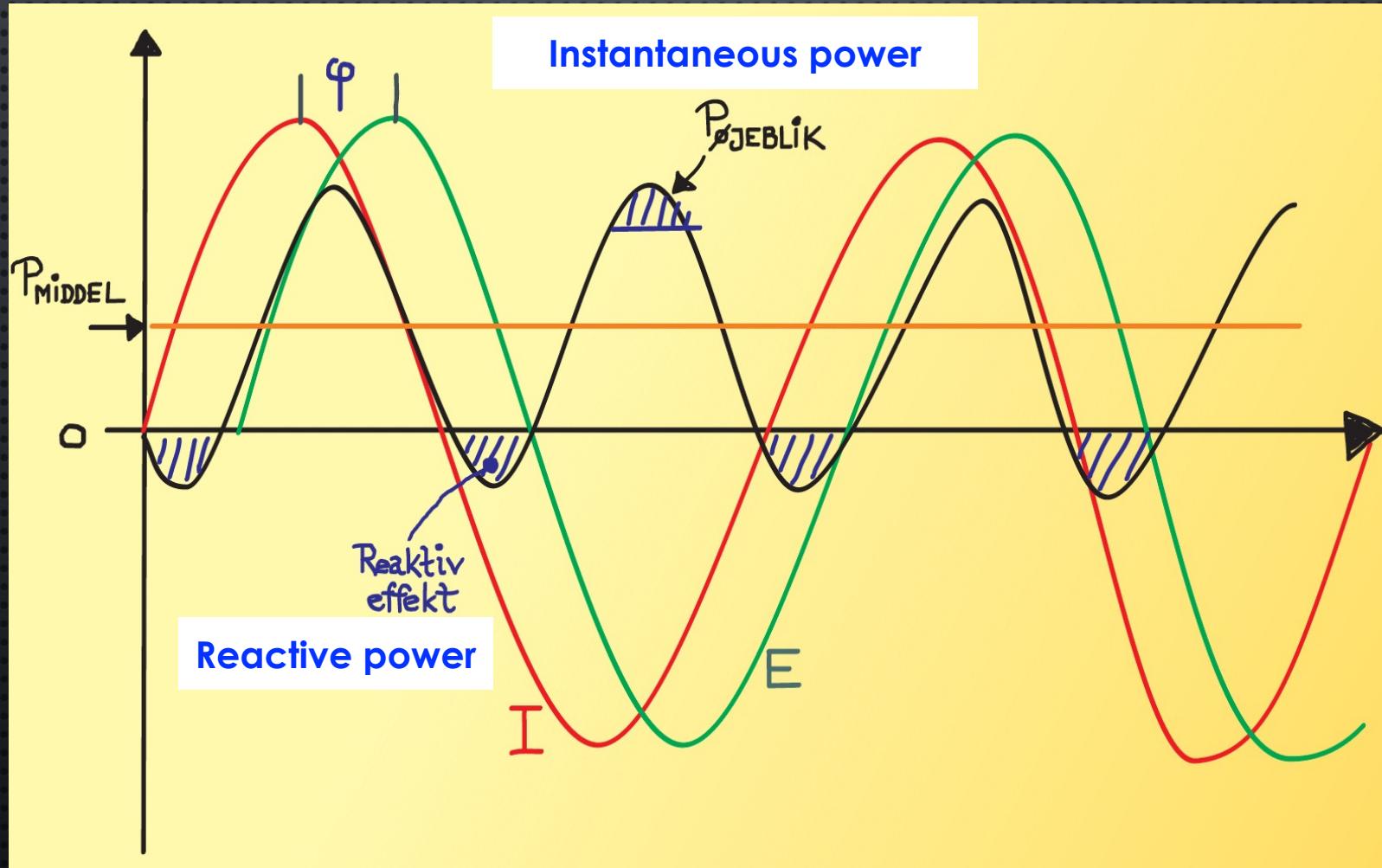
## Instantaneous power V.S. Average power



# Power Calculations in KSN with Lossy Cables
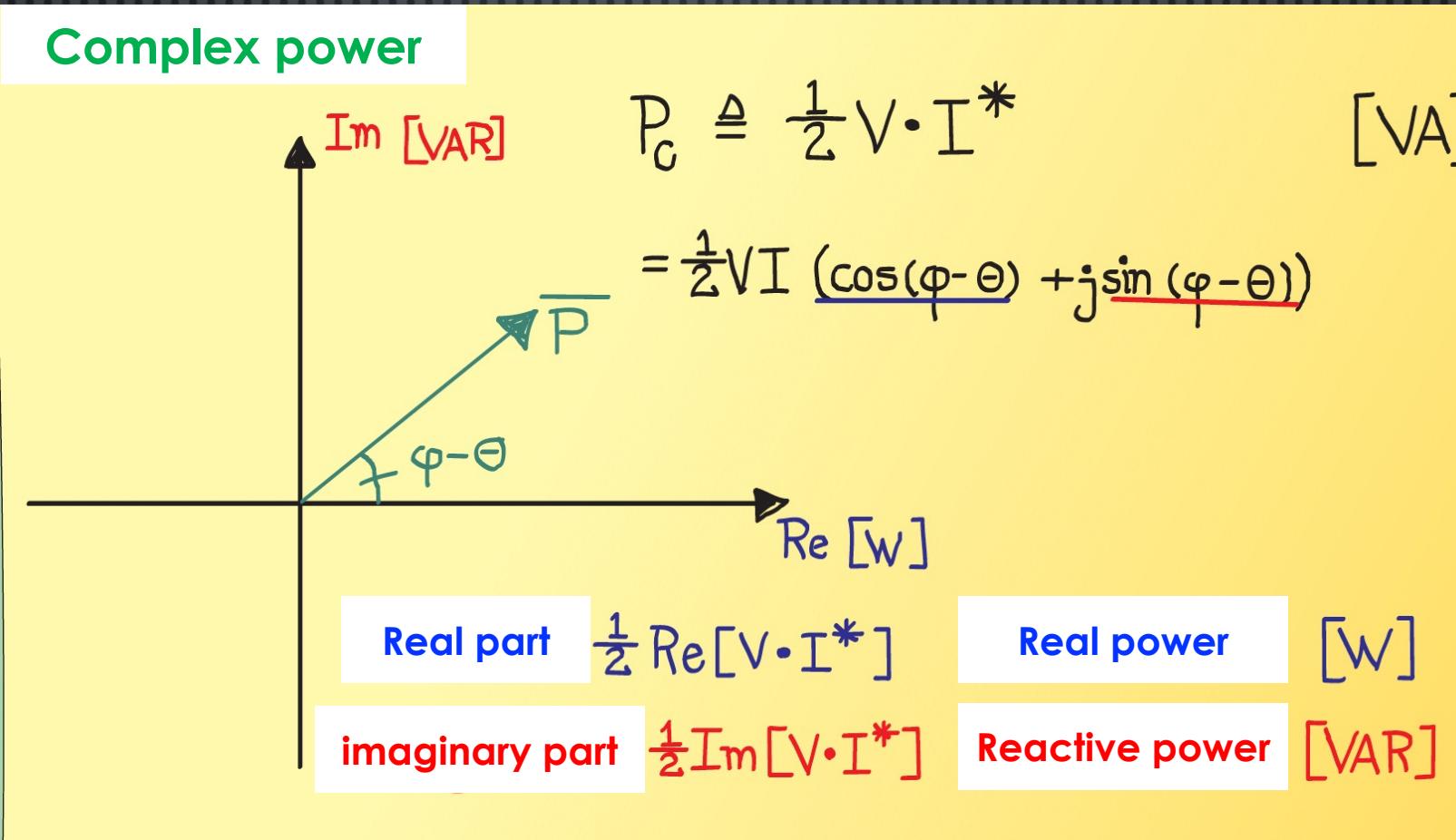
## Instantaneous power V.S. Average power




# Power Calculations in KSN with Lossy Cables

Instantaneous power V.S. Average power



# Power in an Impedance Load (KSN)

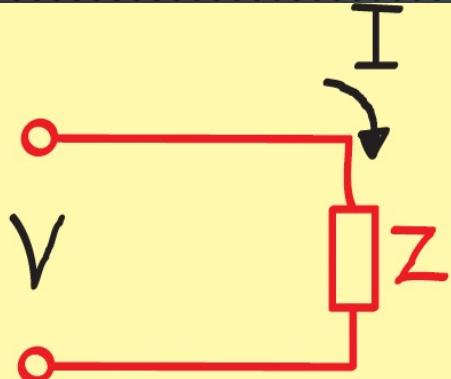

$$I = \frac{V}{Z}$$

$$\begin{aligned} P_{\text{MD}} &= \frac{1}{2} \operatorname{Re}[V \cdot I^*] = \frac{1}{2} \operatorname{Re}[V \cdot V^* \frac{1}{Z^*}] \\ &= \frac{1}{2} \operatorname{Re}[|V|^2 \cdot \frac{Z}{|Z|^2}] \\ &= \frac{1}{2} |V|^2 \cdot \operatorname{Re}[Z] = \frac{1}{2} |I|^2 \cdot \operatorname{Re}[Z] \end{aligned}$$

**Rules for conjugate calculations**

$$Z \cdot Z^* = |Z|^2 = |Z^2|$$

$$\frac{|Z_1|}{|Z_2|} = \left| \frac{Z_1}{Z_2} \right|$$

$$\frac{1}{Z^*} = \frac{Z}{|Z|^2}$$

$$z = a + jb$$

$$\left( \frac{Z_1}{Z_2} \right)^* = \frac{Z_1^*}{Z_2^*}$$

$$z^* = a - jb$$

$$(Z_1 + Z_2)^* = Z_1^* + Z_2^*$$

$$|Z| = \sqrt{a^2 + b^2}$$

$$z = a + jb$$

$$z^* = a - jb$$

$$M \angle \varphi = M(\cos \varphi + j \sin \varphi)$$

$$\begin{aligned} M \angle -\varphi &= M(\cos -\varphi + j \sin -\varphi) \\ &= M(\cos \varphi - j \sin \varphi) \end{aligned}$$

$$|Z| = M = \sqrt{a^2 + b^2}$$

$$\angle Z = \varphi = \arctg \frac{b}{a}$$


$$Z \cdot Z^* = a^2 + b^2 = M^2 = |Z|^2 = |Z^2|$$

$$Z = \frac{|Z|^2}{Z^*}$$

# Power Transmission (KSN)
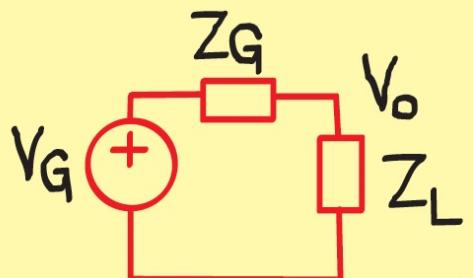
## Power calculation (KSN)


$$P = \operatorname{Re}[V \cdot I^*] \frac{1}{2} \text{ [W]}$$



$$\begin{aligned} P_{Z_L} &= \operatorname{Re}[V \cdot I^*] \frac{1}{2} \\ &= \operatorname{Re}\left[V_G \cdot \frac{Z_L}{Z_G + Z_L} \cdot V_G^* \cdot \frac{1}{(Z_G + Z_L)^*}\right] \frac{1}{2} \\ &= \frac{|V_G|^2}{|Z_G + Z_L|^2} \cdot \operatorname{Re}[Z_L] \frac{1}{2} \text{ [W]} \end{aligned}$$

Konjugeret tilpasning for  $Z_L = Z_G^*$ . Dette  
giver maximal effekt afsat i  $Z_L$ .

# Power Transmission (KSN)

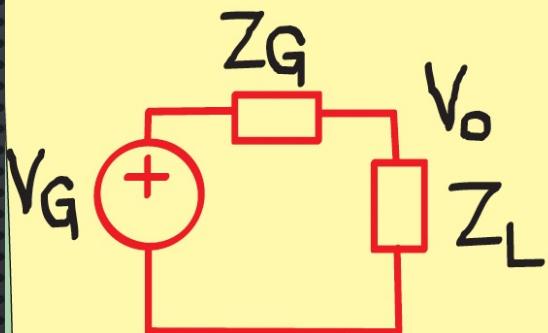

$$P_A = P_{ZL} \Big|_{ZL=ZG^*} = \frac{|V_G|^2}{|2\operatorname{Re}[Z_G]|^2} \cdot \operatorname{Re}[Z_G] \frac{1}{2}$$
$$= \frac{|V_G|^2}{4\operatorname{Re}[Z_G]} \frac{1}{2} \text{ [W]}$$

Eller:

$$P_A = \frac{|V_o|^2}{|Z_L|^2} \cdot \operatorname{Re}[Z_L] \frac{1}{2}$$
$$= \frac{|V_o|^2}{|Z_G|^2} \cdot \operatorname{Re}[Z_G] \frac{1}{2} \text{ [W]}$$

Konjugeret tilpasning for  $Z_L = Z_G^*$ . Dette  
giver maximal effekt afsat i  $Z_L$ .