
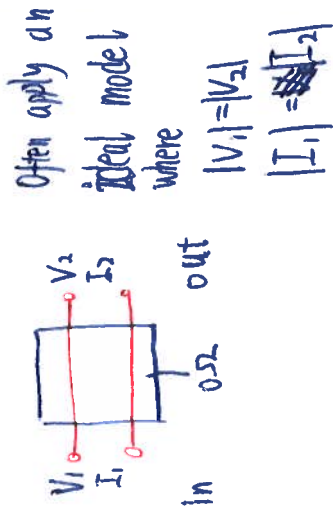


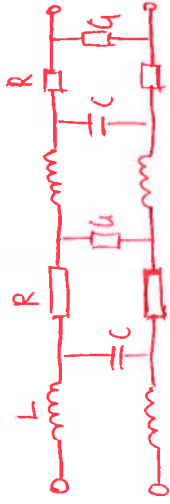(1) Transmission line

We investigate current and voltage on a transmission line:



Cable model 1 (general)



A system with distributed parameters


Primary cable constants:

$$L \left[\frac{H}{m} \right] \quad R \left[\frac{\Omega}{m} \right]$$

$$C \left[\frac{F}{m} \right] \quad G \left[\frac{S}{m} \right]$$

The same symbols L, C, R, G to the circuit theory

Cable model 2 (infinite small)

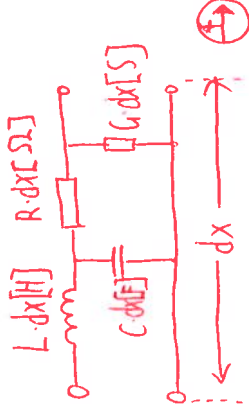


Positive x direction

Symbol



Cable model 3 (lossless)

lossless: $R = G = 0$

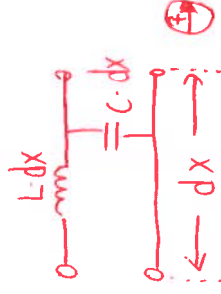

(2) Telegraph equation

Voltage over dx [m]

(Lenz's law)

$$dV = -\frac{\partial \phi}{\partial t} = -L \cdot dx \frac{\partial I}{\partial t}$$

$$\frac{\partial V}{\partial x} = -L \frac{\partial I}{\partial t} \quad (1)$$

For currents: $I + dI$

$\frac{1}{C}$ Q reduction leads to dI increase

$$dI = -\frac{\partial Q}{\partial t} = -C dx \frac{\partial V}{\partial t}$$

$$\frac{\partial I}{\partial x} = -C \frac{\partial V}{\partial t} \quad (2)$$

(1) and (2) are telegraph equations.

$[V(x,t), I(x,t)]$ are functions

Wave equations

Differentiate (1) with x

$$\frac{\partial^2 V}{\partial x^2} = -L \cdot \frac{\partial^2 I}{\partial x \partial t} \quad (3)$$

and differentiate (2) with t

$$\frac{\partial^2 I}{\partial x \partial t} = -C \frac{\partial^2 V}{\partial t^2} \quad (4)$$

(combine (3) and (4))

$$\frac{1}{LC} \frac{\partial^2 V}{\partial x^2} = \frac{\partial^2 V}{\partial t^2} \quad (5)$$

One dimension wave equation

Solutions

The solution of wave equations

can be:

$$V(x,t) = k_1 V_1(x,t) + k_2 V_2(x,t)$$

V_1 and V_2 are solutions.

Any functions with parameters:

$$(t \pm x\sqrt{LC})$$

are solutions.

For example: (different wave forms)

$$V(x,t) = 25 \cdot (t + x\sqrt{LC})$$

$$V(x,t) = 45 \cos[\omega(t - x\sqrt{LC})]$$

$$V(x,t) = u(t - x\sqrt{LC})$$

Propagation speed

$$V = \frac{1}{\sqrt{LC}} \left[\frac{m}{s} \right]$$

are the propagation speed in cable

Light speed in vacuum


$$c \approx 3 \times 10^8 \frac{m}{s}$$

This is the max speed of energy and information propagation.

$$\text{So } V \leq c$$

③ Paradigm model ★

Diagram

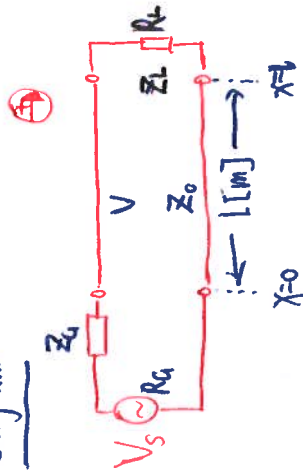

Current and voltage:

$$V(x, t) = V^+(t - \frac{x}{v}) + V^-(t + \frac{x}{v}) \quad [V]$$

$$I(x, t) = I^+(t - \frac{x}{v}) + I^-(t + \frac{x}{v}) \quad [A]$$

$$= \frac{1}{Z_0} [V^+(t - \frac{x}{v}) - V^-(t + \frac{x}{v})] \quad [A]$$

Z_0 is defined:

$$Z_0 = \sqrt{\frac{L}{C}} \quad [\Omega]$$

Characteristic impedance

We can find (when wave equation is linear)

$$I^+ = \frac{V^+}{Z_0} \quad I^- = -\frac{V^-}{Z_0} \quad [A]$$

$$\Rightarrow Z_0 = \frac{V^+}{I^+} = -\frac{V^-}{I^-} \quad [\Omega]$$

I_t is also defined:

$$K_L = \frac{V^-}{V^+} = -\frac{I^-}{I^+} \quad [.]$$

Reflection coefficient

I_t can also be calculated

by:

$$K_L = \frac{Z_L - Z_0}{Z_L + Z_0} \quad [.]$$

$V^+(x, t)$ and $I^+(x, t)$

are incident wave

$V^-(x, t)$ and $I^-(x, t)$


are reflective wave

Propagation on cable

We see from incident

wave:
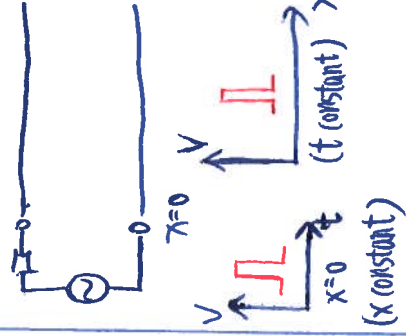
$$V(x, t) = V^+(t - \frac{x}{v}) \quad [V]$$



V^+ propagate to right

V^- propagate to left

Reflection

We have

$$V^- = K_L V^+$$

$$I^- = -K_L I^+$$

Summary with K_L and Z_L

Z_L	K_L
0	-1
∞	+1
Z_0	0

$$K_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$