

High-Speed Electronics in Practice

SHUAI ZHANG

SELMA LAGERLOFS VEJ 312

9220 AALBORG ØST

(sz@es.aau.dk)

High-Speed Electronics in Practice

MM7. Impulse Propagation on Cables and Telegraph Equation


IMPULSE PROPAGATION ON CABLES AND TELEGRAPH EQUATION

Targets:

1. Read “Grundlæggende Transmissionsledningsteori” (Page 1-22)
(before or after the lecture)
2. Be able to calculate with reflection map (lecture)
3. Finish the exercise (after the lecture)

Questions


Water container

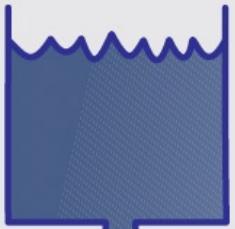

10 km



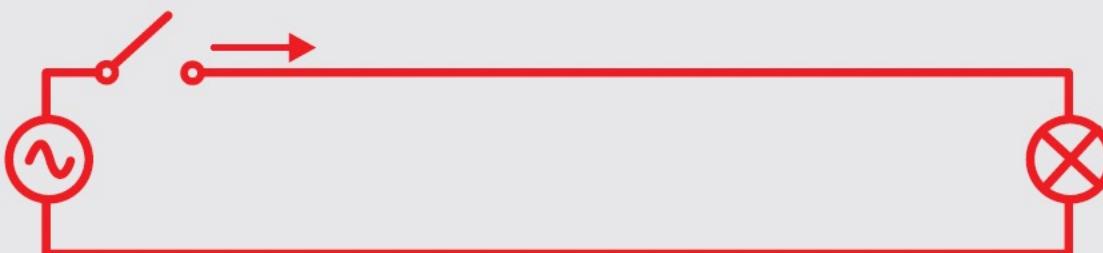Press the water with the speed of 1200 m/s. Delay for around 8 s



220 V
50 Hz


Pære
60 W

How much current runs in the cable, right after turn on the switch?

Transmission Line

Blackboard (1)

Parallel cable

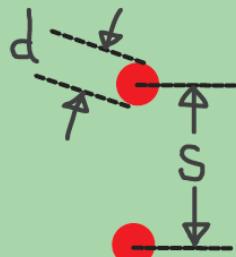

PARALLEL
LEDER

$$\epsilon = \epsilon_0 \cdot \epsilon_r \quad [\text{F/m}]$$

$$\mu = \mu_0 \cdot \mu_r \quad [\text{H/m}]$$



$$L = \frac{\mu}{\pi} \cdot \ln\left(\frac{2s}{d}\right) \quad [\text{H/m}]$$

$$C = \pi \cdot \epsilon \cdot \frac{1}{\ln\left(\frac{2s}{d}\right)} \quad [\text{F/m}]$$

$$Z_0 = \frac{120}{\sqrt{\epsilon_r}} \cdot \ln\left(\frac{2s}{d}\right) \quad [\Omega]$$


(for $\mu_r=1$)
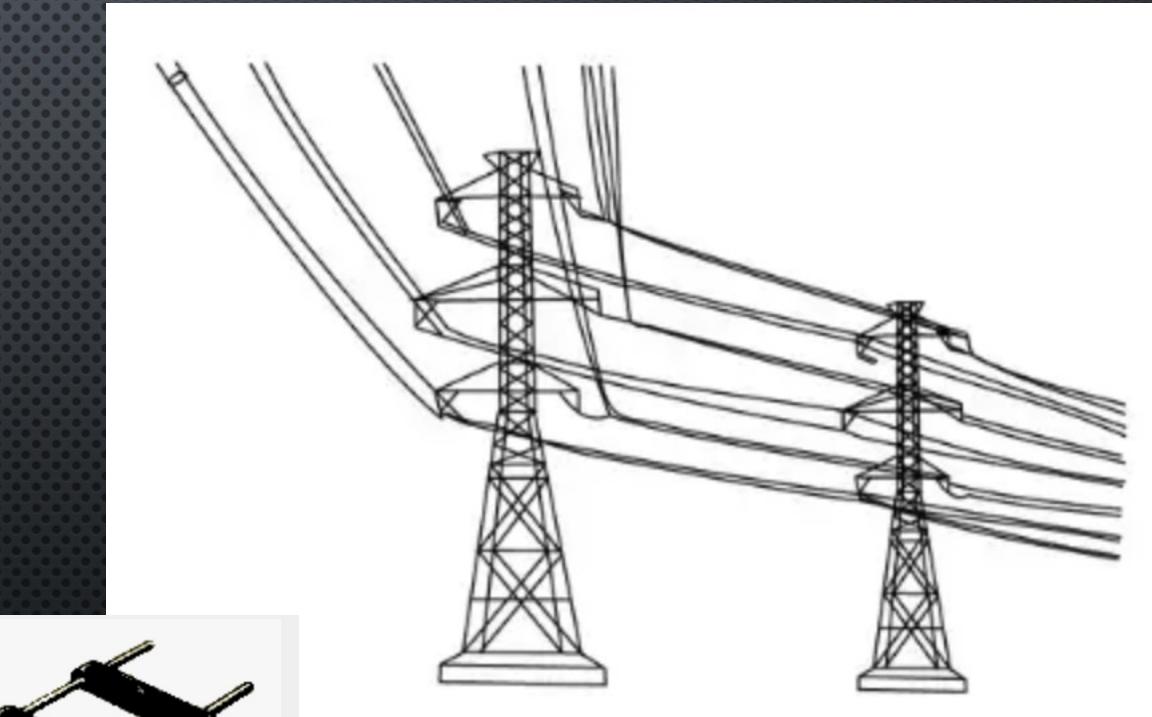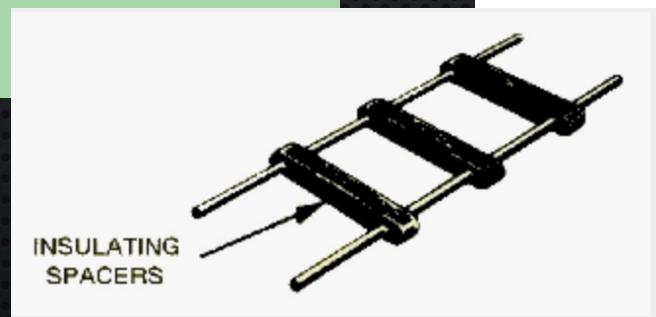
$$V = \frac{1}{\sqrt{\mu \cdot \epsilon}} \quad [\text{m/s}]$$



Transmission Line

Coaxial cable

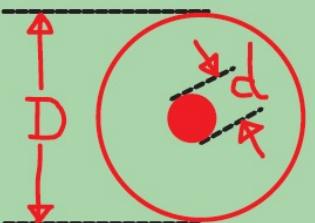

KOAXIAL
KABEL

$$L = \frac{\mu}{2\pi} \cdot \ln\left(\frac{D}{d}\right) \quad [\text{H/m}]$$

$$C = 2\pi \cdot \epsilon \cdot \frac{1}{\ln\left(\frac{D}{d}\right)} \quad [\text{F/m}]$$


$$Z_0 = \frac{60}{\sqrt{\epsilon_r}} \cdot \ln\left(\frac{D}{d}\right) \quad [\Omega]$$

(for $\mu_r = 1$)

$$v = \frac{1}{\sqrt{\mu \cdot \epsilon}} \quad [\text{m/s}]$$



$$\epsilon = \epsilon_0 \cdot \epsilon_r \quad [\text{F/m}]$$
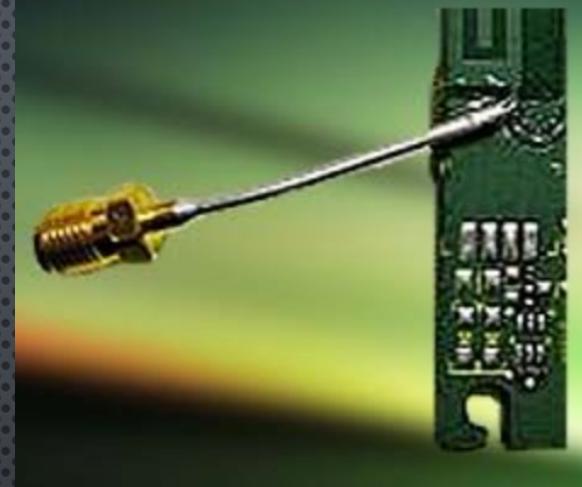
$$\mu = \mu_0 \cdot \mu_r \quad [\text{H/m}]$$



Transmission Line

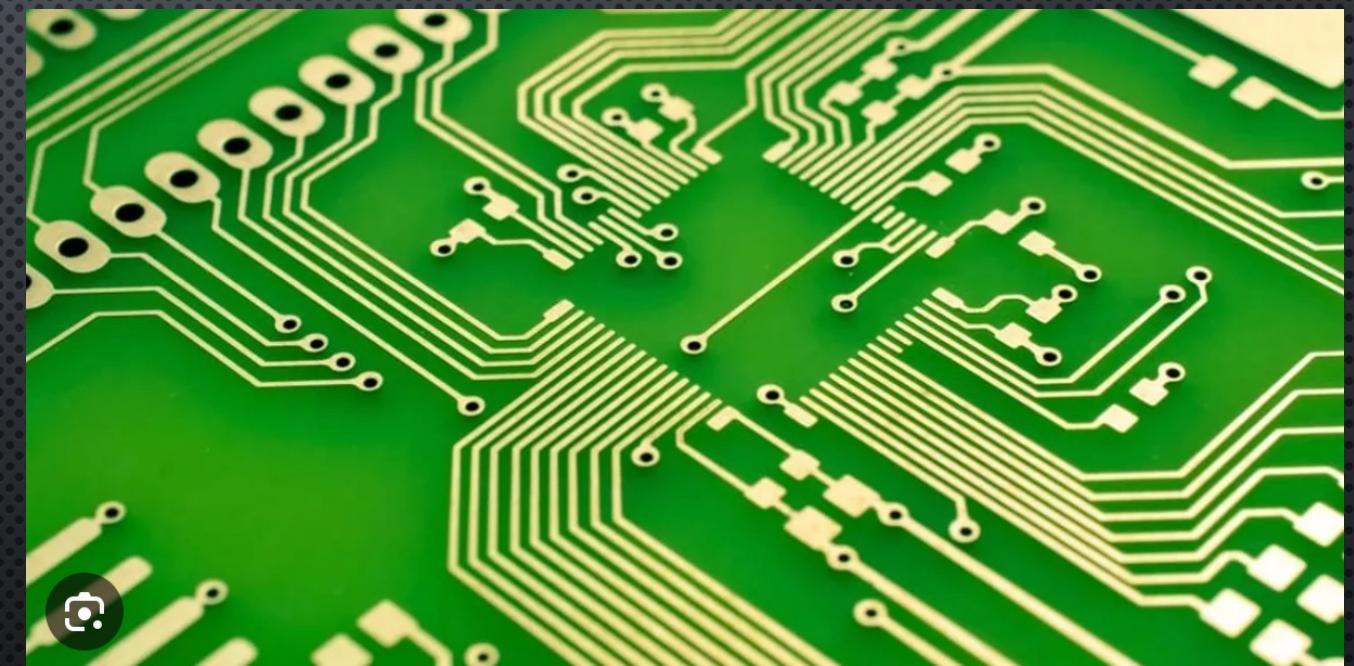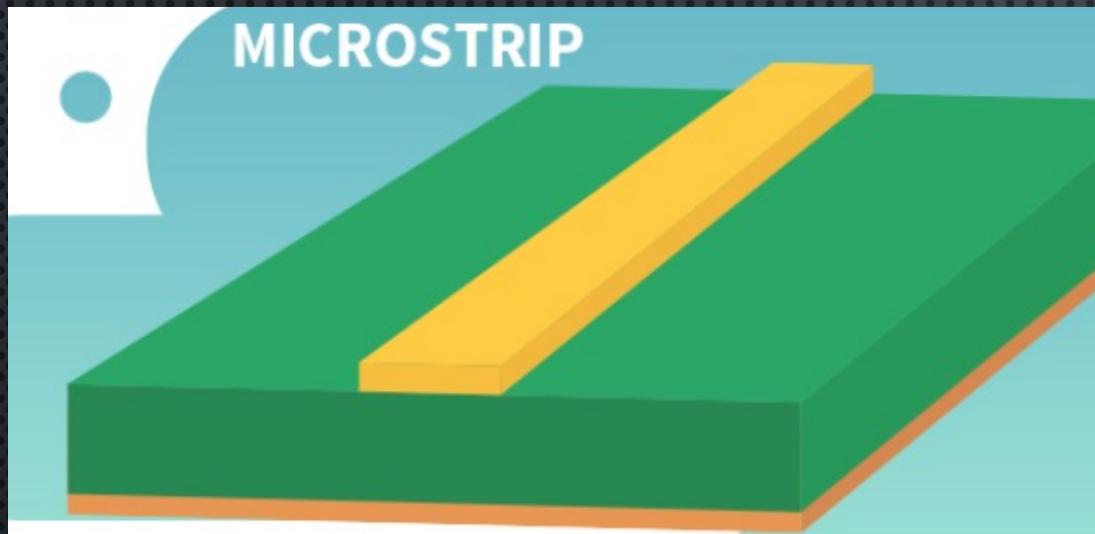Common transmission lines on PCB-Microstrip line






7


cheap solution

Transmission Line

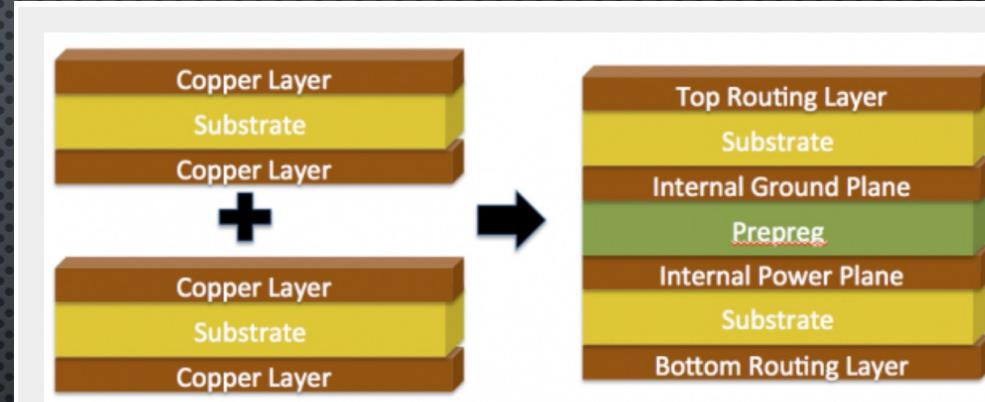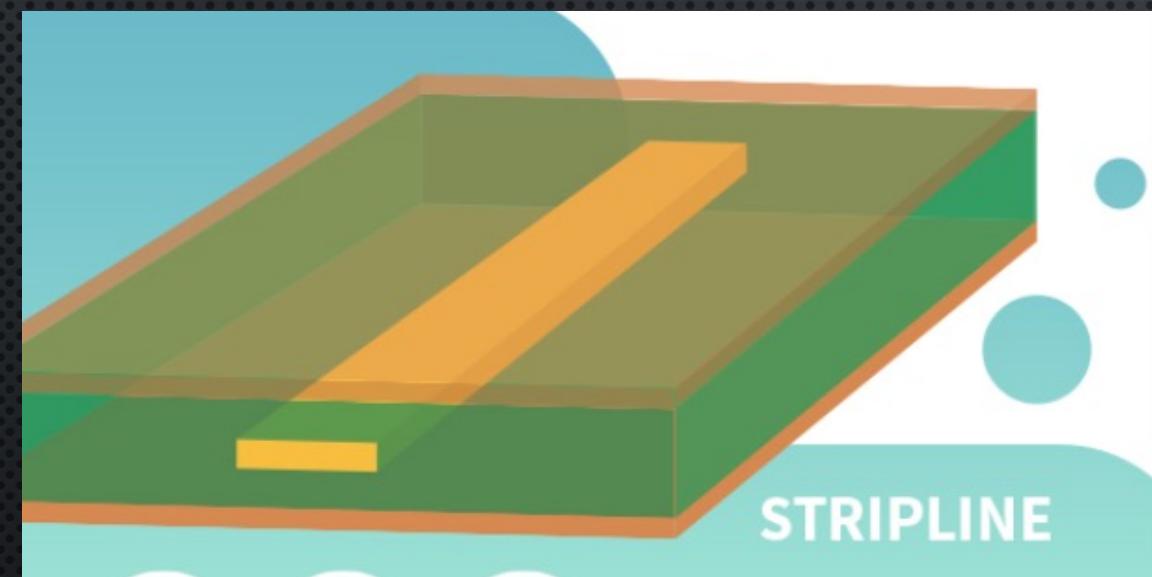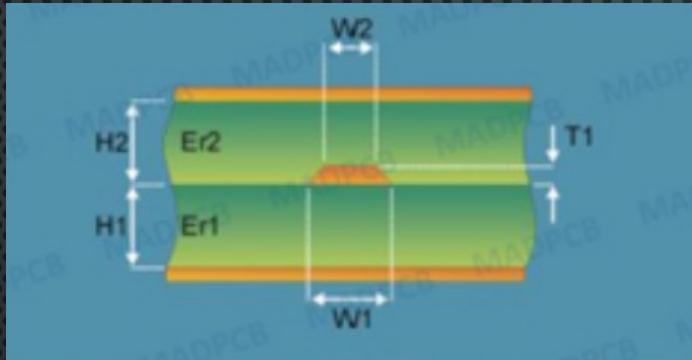Common transmission lines on PCB PCB-Strip line



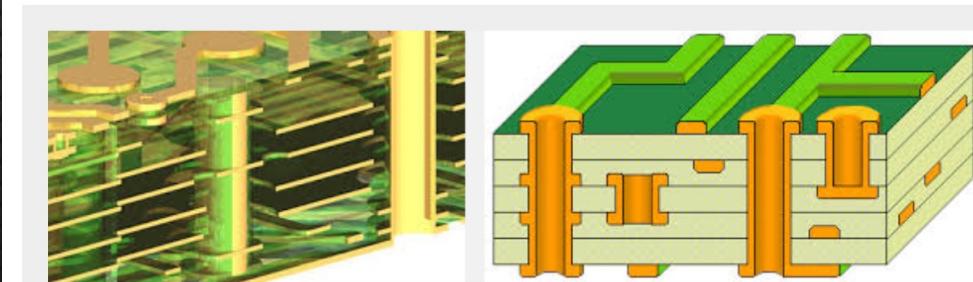— Layers of copper+core are bonded together...




— Different types of vias


Transmission Line

Common transmission lines on PCB-CPW and CPWG

Coplanar waveguide (CPW)

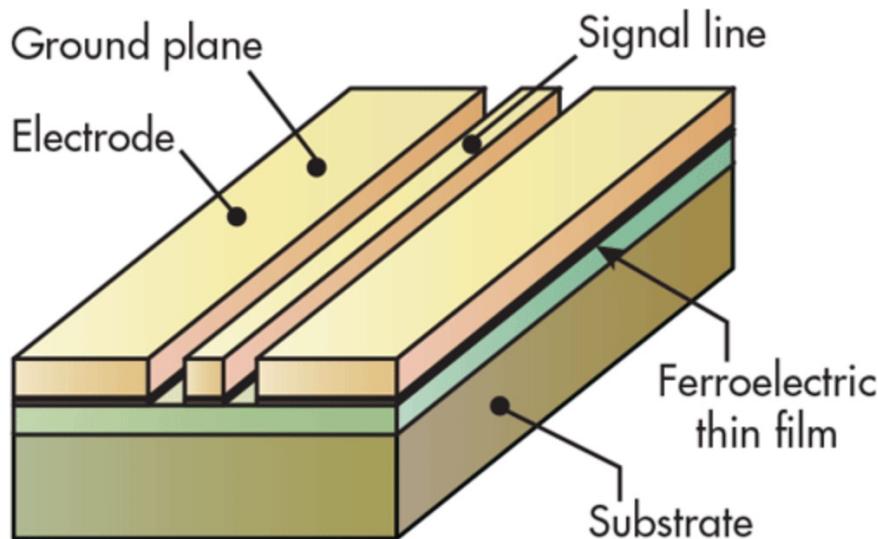


Coplanar waveguide grounded (CPWG)

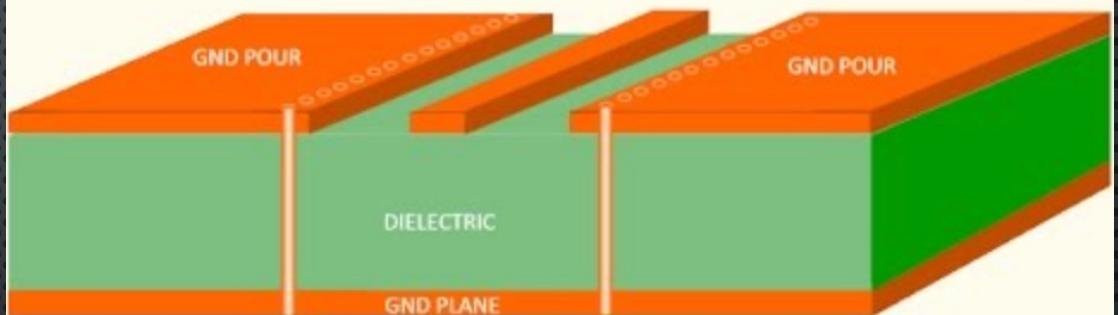

Single Strip Coplanar Waveguide Grounded (CPWG)
1 of 5 Configurations


Very popular in practical applications

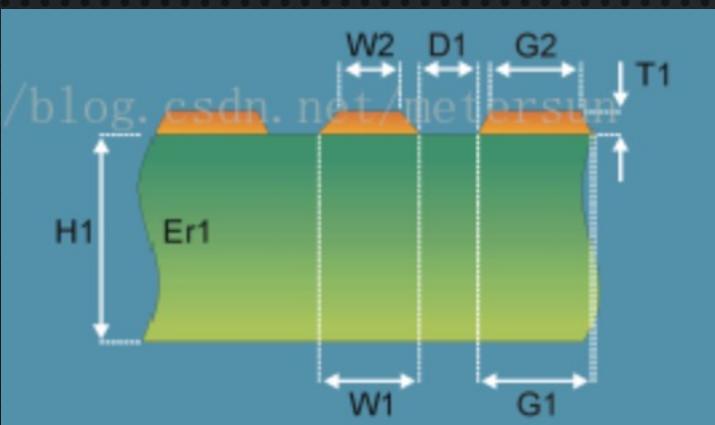

Telegraph Equations and Wave Equations

Blackboard (2)

Model for cable

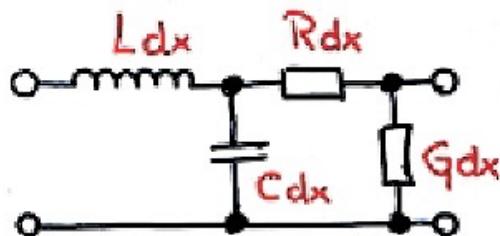


Telegraph equation

Lossless $R=G=0$

$$\frac{\partial V}{\partial x} = -L \cdot \frac{\partial I}{\partial t}$$

$$\frac{\partial I}{\partial x} = -C \cdot \frac{\partial V}{\partial t}$$
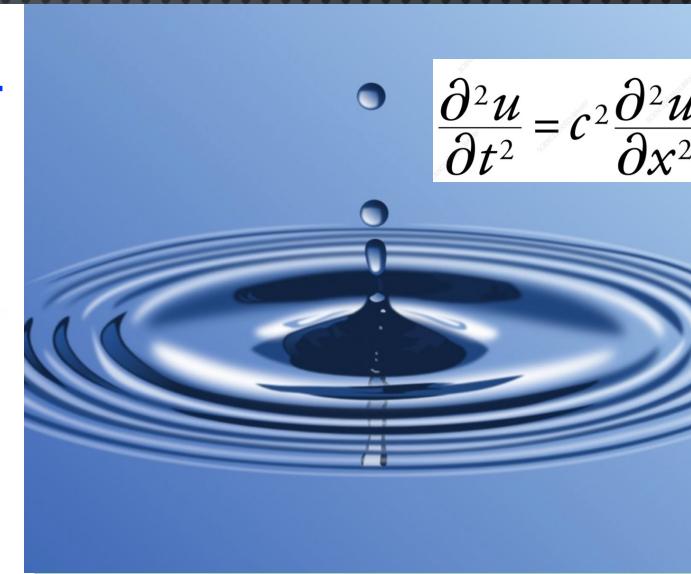
$$\frac{\partial^2 u}{\partial t^2} = c^2 \frac{\partial^2 u}{\partial x^2}$$



Wave equation

Lossless $R=G=0$ $\frac{\partial^2 V}{\partial x^2} = \frac{1}{v^2} \frac{\partial^2 V}{\partial t^2}$

$$\frac{\partial^2 I}{\partial x^2} = \frac{1}{v^2} \frac{\partial^2 I}{\partial t^2}$$

Solutions

$$V = V^+(t - \frac{x}{v}) + V^-(t + \frac{x}{v})$$

$$I = I^+(t - \frac{x}{v}) + I^-(t + \frac{x}{v})$$

$$I = \frac{1}{Z_0} (V^+(t - \frac{x}{v}) - V^-(t + \frac{x}{v}))$$




$$V = \frac{1}{\sqrt{LC}} \left[\frac{m}{s} \right]$$
$$Z_0 = \sqrt{\frac{L}{C}} [\Omega]$$

$$K_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{V^-}{V^+} = -\frac{I^-}{I^+}$$

Paradigm Model


Blackboard (3)

Reflection Diagram

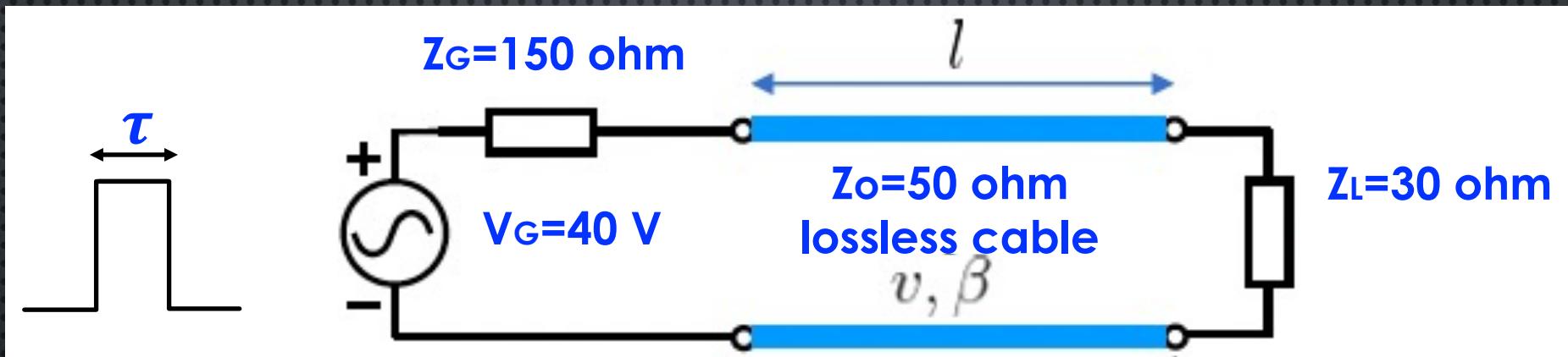


Determine the current and voltage on the Z_L

Reflection Diagram

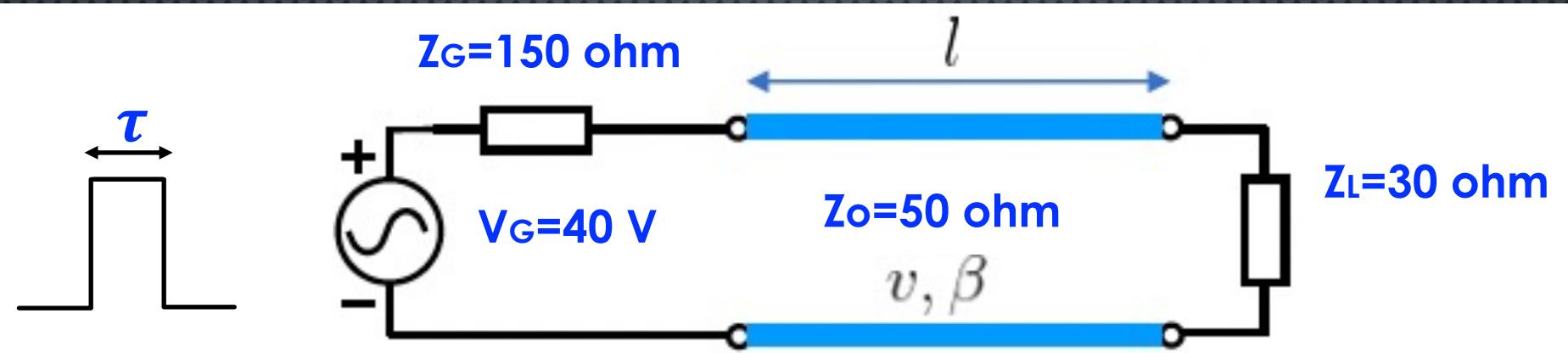

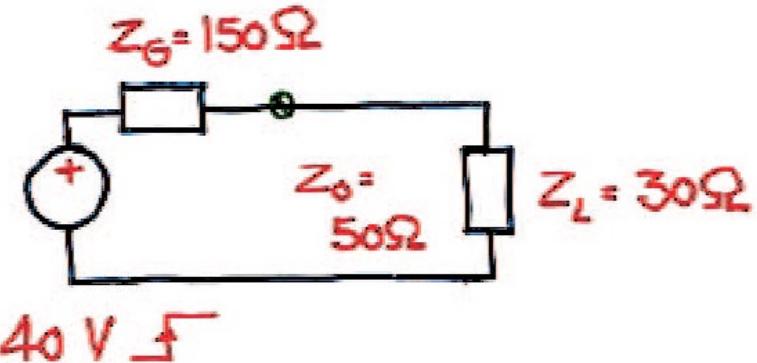
There are many ways
to calculate it.
First, we can utilize
circuit theory.



$$V_S = 40 \cdot \frac{30}{150+30} = \frac{1200}{180} = \frac{20}{3} \text{ V} \quad (6,67 \text{ V})$$

$$I_S = 40 \cdot \frac{1}{150+30} = \frac{40}{180} = \frac{4}{18} \text{ A} \quad (0,22 \text{ A})$$

Reflection Diagram

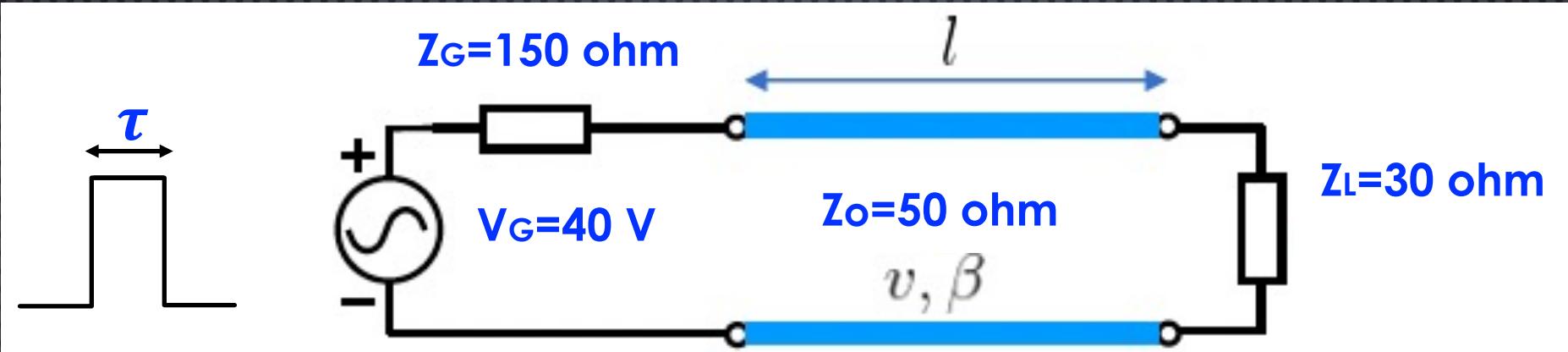

There are many ways to calculate it. We can also apply transmission line theory that gives more details.



Start:

$$V^+ = 40 \cdot \frac{50}{150+50} = \frac{2000}{200} = 10 \text{ V}$$

$$I^+ = 40 \cdot \frac{1}{150+50} = \frac{40}{200} = 0,2 \text{ A}$$


$$K_G = \frac{150 - 50}{150 + 50} = +\frac{1}{2}$$
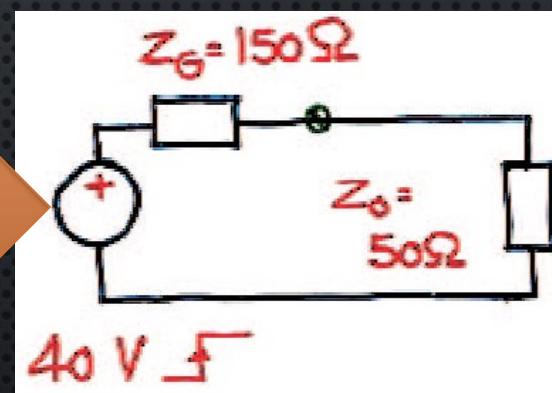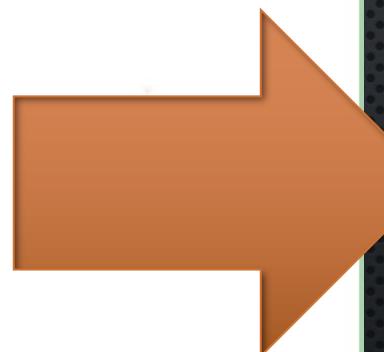
$$K_L = \frac{30 - 50}{30 + 50} = -\frac{1}{4}$$



Reflection map


Reflection Diagram

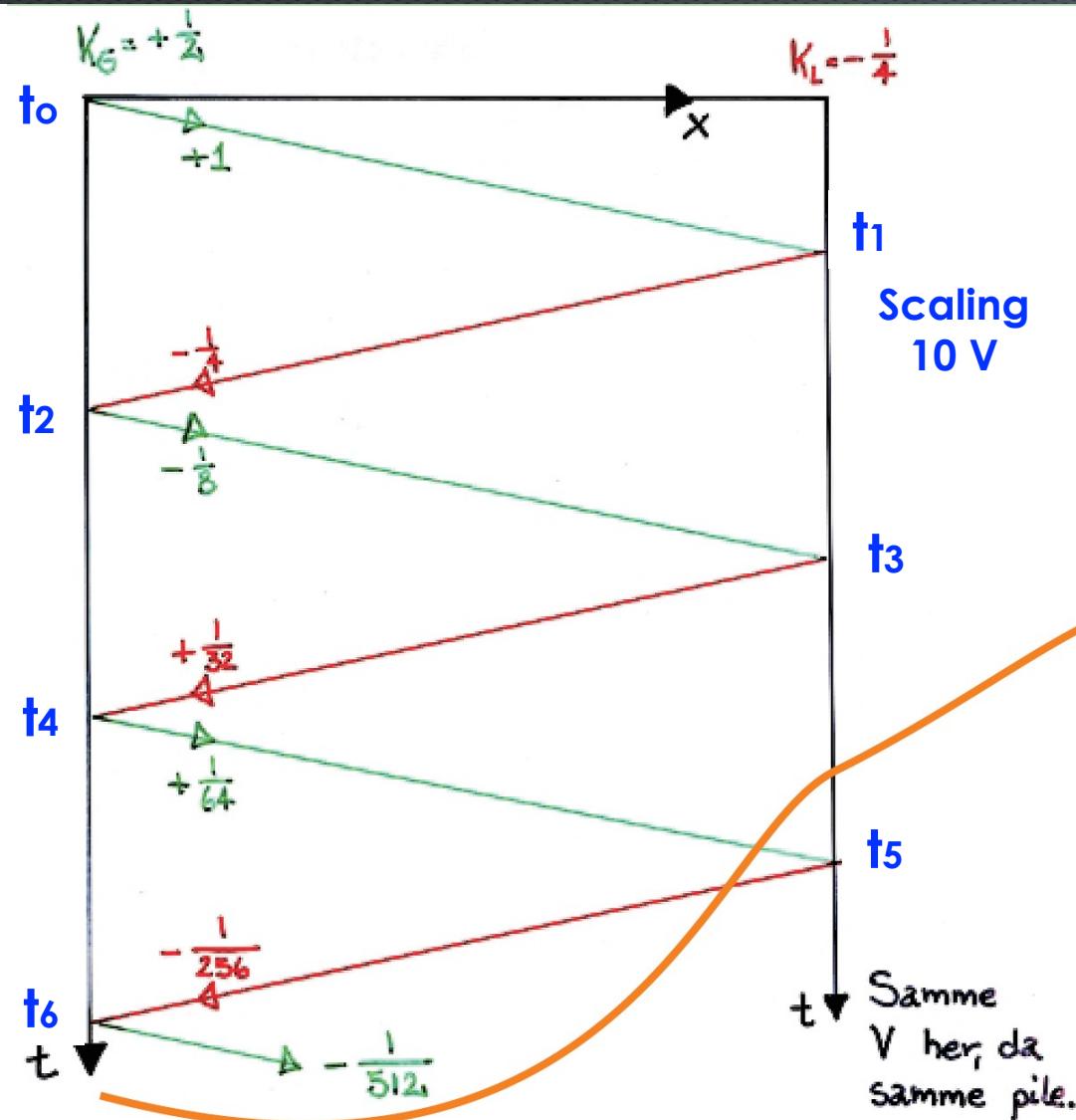

$$\begin{aligned}
 V_{\text{TOTAL}} @ S &= 10 \cdot \\
 &1 + (-\frac{1}{8}) + \frac{1}{2}(-\frac{1}{4}) + \frac{1}{2}(-\frac{1}{4})^2 + (\frac{1}{2})^2(-\frac{1}{4})^2 + \dots \\
 &= \left(\sum_{n=0}^{\infty} (-\frac{1}{8})^n + (-\frac{1}{4}) \sum_{n=0}^{\infty} (-\frac{1}{8})^n \right) \cdot 10 = \frac{3}{4} \cdot \frac{5}{3} \cdot 10 = \frac{25}{3} \text{ V}
 \end{aligned}$$

Reflection map


Reflection Diagram

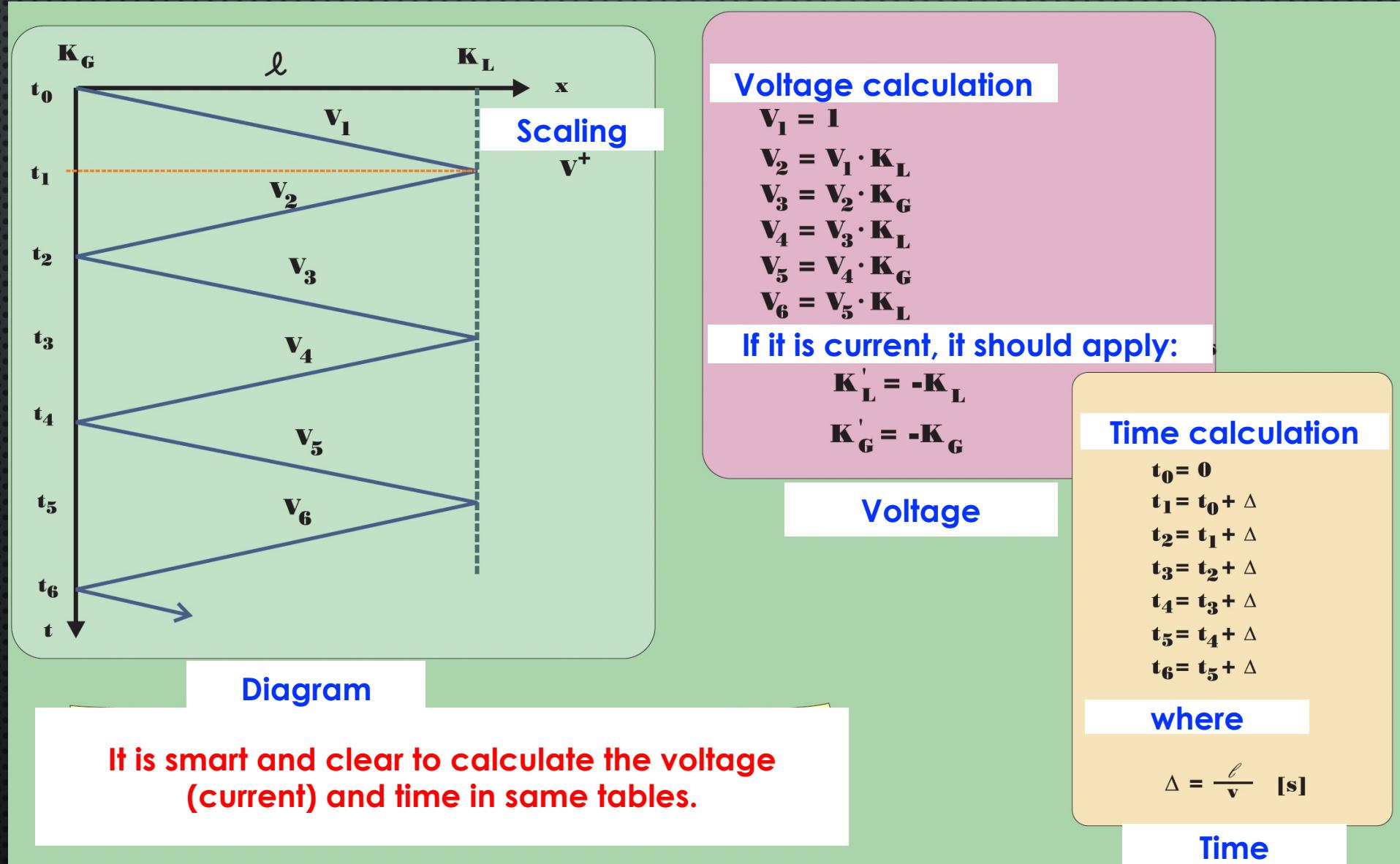



Reflection Diagram

Stick diagram

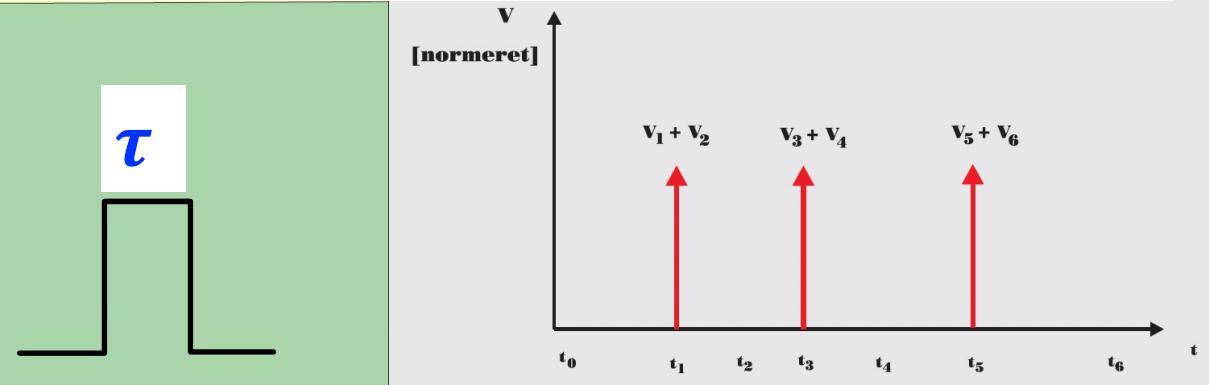Calculate the curve form with stick diagram



Make the wave leading edge with stick

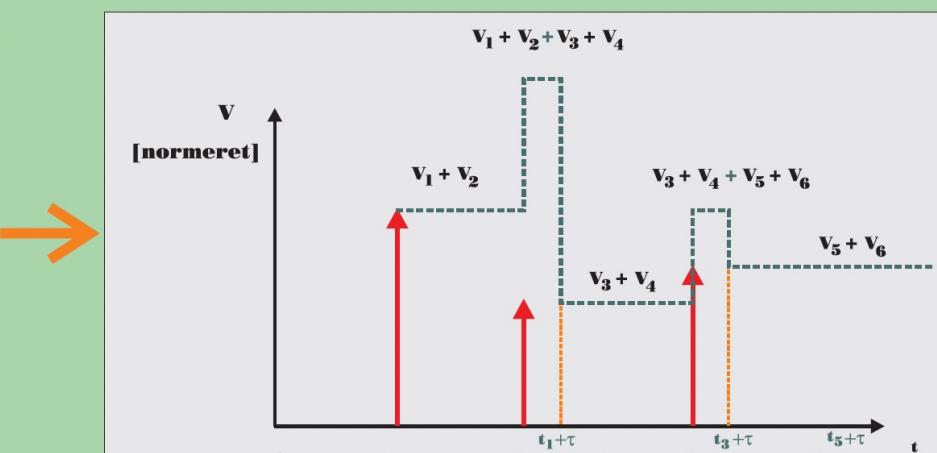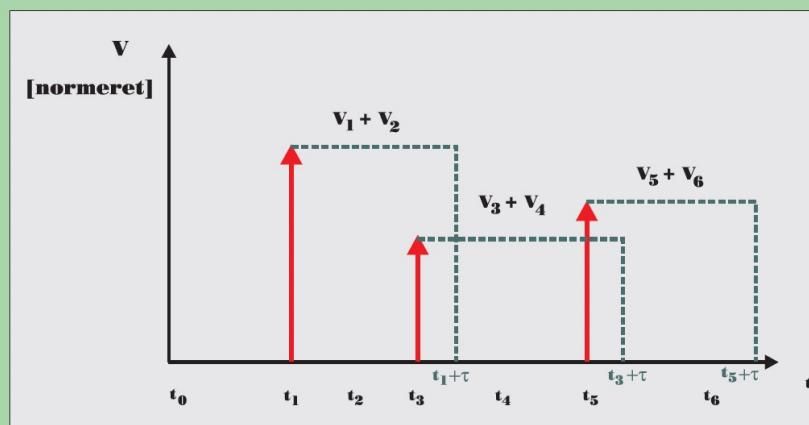

Extend stick to full pulse width

Sum the impulse overlap part

Reflection Diagram

1. Calculate cable parameters. We should have speed v and characteristic impedance Z_0 . Identify generator voltage, generator impedance and load impedance.
2. Determine the first incident signal. Calculate K_L and K_G . If it is current, remember to reverse the sign of the reflection coefficients.
3. Calculate the important time points. This is the time of the wave propagation on the cable, as well as the times of the leading edge of an impulse signal.
4. Draw the reflection map for the leading edge of the signals.
5. Make a "stick" graph for each signal. Calculate the voltage or currents.
6. Extend the sticks to the entire pulse and sum the signals if they overlap.
7. Multiply the entire graph by the scaling factor (the first incident V or I).