

Exercise 11.1


We consider a transmission line setup where the load Z_L consists of $95\ \Omega$ in series with $24\ \text{pF}$. The characteristic impedance of the cable is $50\ \Omega$, and it is lossless. The frequency is $100\ \text{MHz}$.

In this exercise, we need to determine the standing wave curve for the current. We assume the incident current wave is $1\ \text{A}$ (peak).

- Calculate the load impedance and express it in rectangular form.
- Calculate K_L and express it in polar form.
- Calculate the maximum and minimum currents on the cable.
- Calculate the current through Z_L .
- Calculate the distance from the load to the first current maximum, given in "wavelengths," and sketch the standing wave curve from the load to half a wavelength towards the generator.

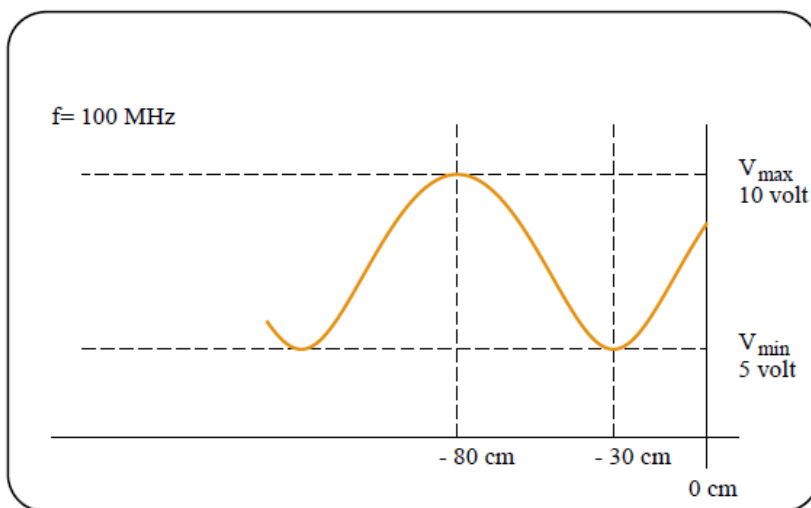Exercise 11.2

On a lossless cable with a characteristic impedance of $50\ \Omega$, the following standing wave curve for voltage has been measured. The distance from the load to the first voltage minimum is $30\ \text{cm}$, and the distance from the load to the first voltage maximum is $80\ \text{cm}$. The maximum voltage is $10\ \text{V}$ (peak), and the minimum voltage is $5\ \text{V}$ (peak). The frequency is $100\ \text{MHz}$.



- Determine the standing wave ratio (SWR), the magnitude of the reflection coefficient K_L , and the wavelength on the cable.
- Determine K_L and the value of the load impedance Z_L .
- Provide two possible realizations of Z_L (one in series and one in parallel).
- Calculate the amplitude of the incident voltage wave and the amplitude of the voltage across the load.